
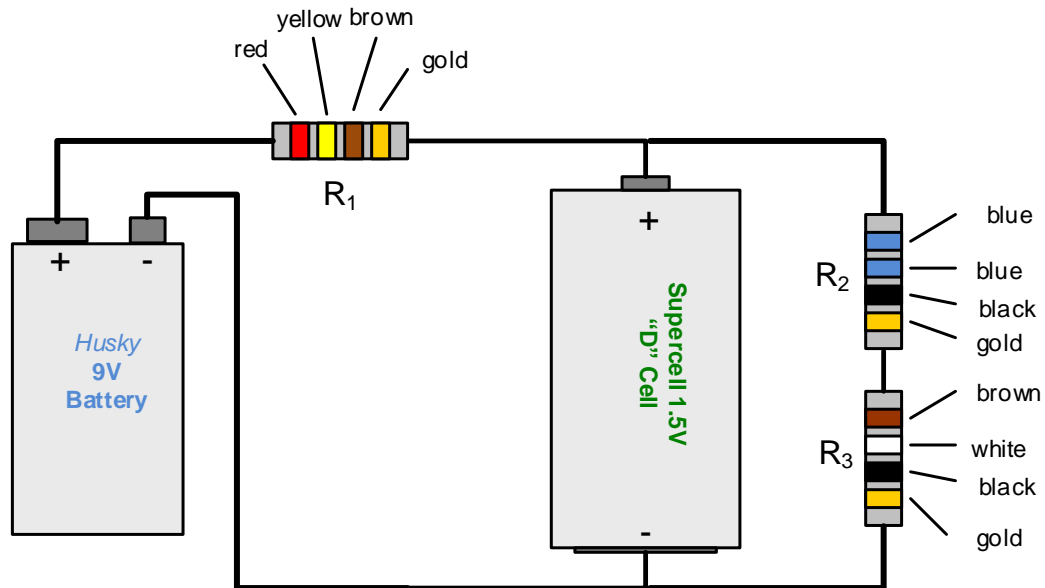


Homework Assignment 1 **SOLUTION**
Due: Friday, Sept. 6, 2019

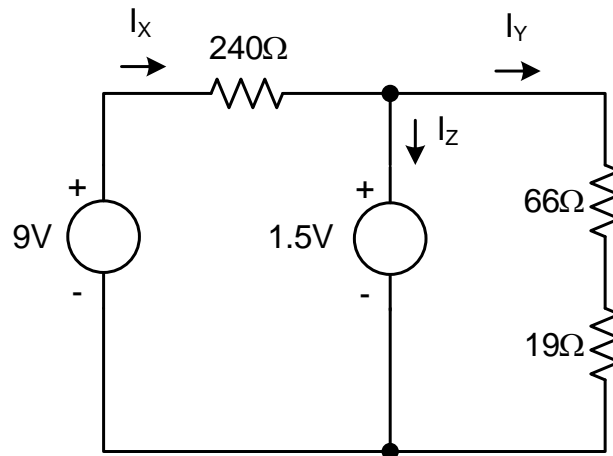1. (25) Two batteries and three resistors are connected as shown below. a) Does conventional current enter or leave the positive terminal of the 9 V battery? b) Do electrons enter or leave the positive terminal of the 9 V battery? c) Does the 9 V battery develop or dissipate power? d) Does conventional current enter or leave the positive terminal of the 1.5 V battery? e) What is the power for the 1.5 V battery? (Use the passive sign convention.) f) Find the power for each of the resistors.



Solution. The simplified circuit is as follows.



a) Conventional current leaves the positive terminal of the 9V battery because

$$I_X = \frac{9V - 1.5V}{240\Omega} = 31.25 \text{ mA}.$$

b) Electrons enter the positive terminal of the 9V battery (opposite to the flow of conventional current).

c) The 9V battery develops power because

$$P_{9V} = -(9V)(31.25 \text{ mA}) = -281.25 \text{ mW}.$$

d) We can find the current in the 1.5 battery as follows.

$$I_Y = \frac{1.5V}{66\Omega + 19\Omega} = 20.0 \text{ mA (OHM)}$$

$$I_Z = I_X - I_Y = 11.25 \text{ mA (KCL)}$$

e) The power for the 1.5V battery is

$$P_{1.5V} = (1.5V)(11.25 \text{ mA}) = 16.875 \text{ mW}$$


f) For the resistors,

$$P_{240\Omega} = \frac{7.5V^2}{240\Omega} = 234.37 \text{ mW},$$

$$P_{66\Omega} = (0.02A)^2 66\Omega = 26.4 \text{ mW and}$$


$$P_{19\Omega} = (0.02A)^2 19\Omega = 7.6 \text{ mW}.$$

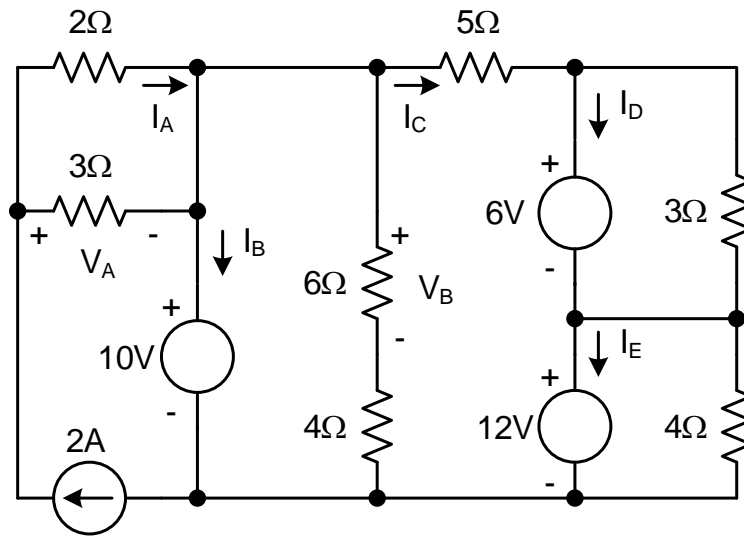2. (25) Consider the resistive circuit below.



- Find V_A , V_B , I_A , I_B , I_C , I_D , and I_E .
- Find the power for each of the sources, using the passive sign convention. Do any of the sources *dissipate* power?

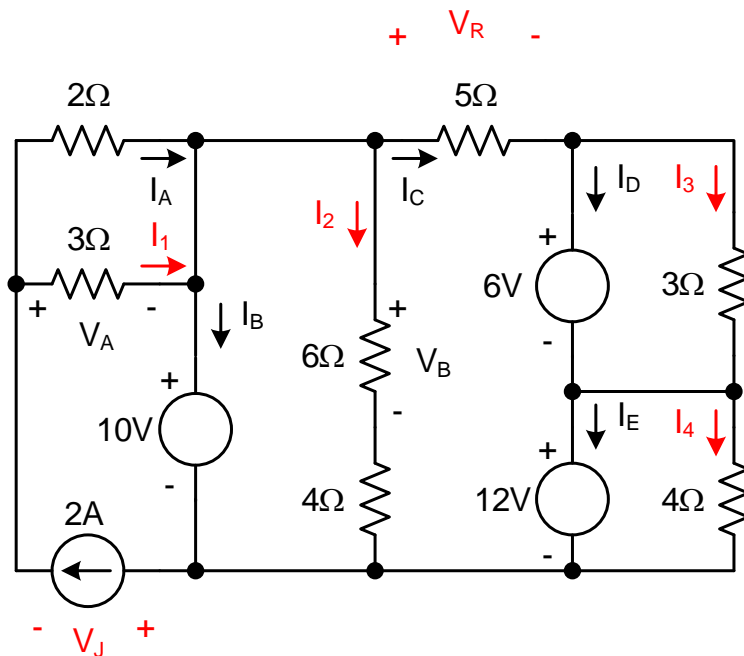Solution. (ad hoc use of KVL, KCL, and Ohm's law)



a. CDR: $I_A = 2A \left(\frac{3\Omega}{2\Omega + 3\Omega} \right) = 1.2 A$

$$\text{CDR: } I_1 = 2A \left(\frac{2\Omega}{2\Omega + 3\Omega} \right) = 0.8 A$$

$$\text{Ohm: } V_A = (0.8A)(3\Omega) = 2.4 V$$

$$\text{KVL: } -10 + V_R + 6 + 12 = 0 \quad V_R = -8 V$$

$$\text{Ohm: } I_C = \frac{-8V}{5\Omega} = -1.6 A$$

$$\text{KVL and Ohm: } I_2 = \frac{10V}{10\Omega} = 1 A$$

$$\text{VDR: } V_B = 10V \left(\frac{6\Omega}{4\Omega + 6\Omega} \right) = 6 V$$

$$\text{KCL: } I_B - I_A - I_1 + I_2 + I_C = 0 \quad I_B = 2.6 A$$

$$\text{Ohm: } I_3 = \frac{6V}{3\Omega} = 2 A$$

$$\text{KCL: } -I_C + I_D + I_3 = 0 \quad I_D = -3.6 A$$

$$\text{Ohm: } I_4 = \frac{12V}{4\Omega} = 3 A$$

$$\text{KCL: } I_E + I_4 - I_3 - I_D = 0 \quad I_E = -4.6 A$$

$$\text{b. KVL: } V_A + 10 + V_J = 0 \quad V_J = -12.4 V$$




$$P_{2A} = (2A)(-12.4V) = -24.8 W$$

$$P_{10V} = (10V)(2.6A) = 26 W \text{ (The 10V source dissipates.)}$$

$$P_{6V} = (6V)(-3.6A) = -21.6 W$$


$$P_{12V} = (12V)(-4.6A) = -55.2 W$$

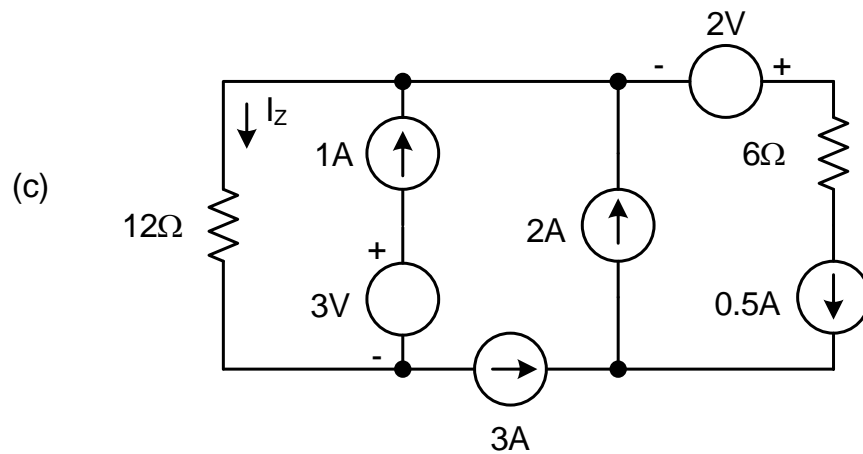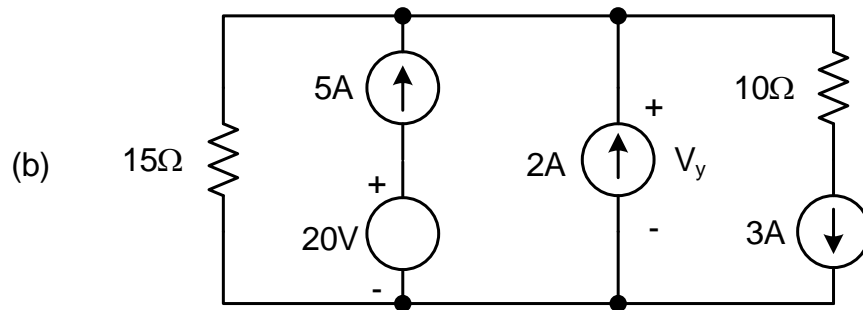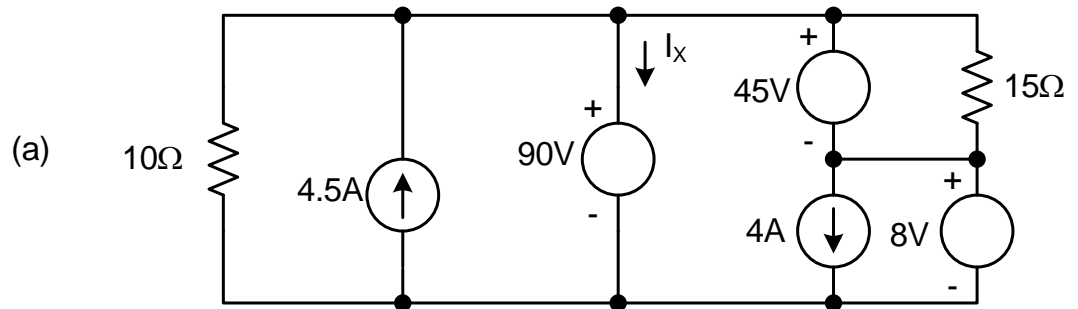3. (25) Consider the following three circuits.
- (a) Is circuit a valid? If it is, find I_x . If not, show a violation of Kirchhoff's laws.
- (b) Is circuit b valid? If so, determine V_y . If not, show a violation of Kirchhoff's laws.
- (c) Is circuit c valid? If so, find I_z . If not, show a violation of Kirchhoff's laws.




Solution.

a. NOT VALID. KVL: $-90 + 45 + 8 \neq 0$

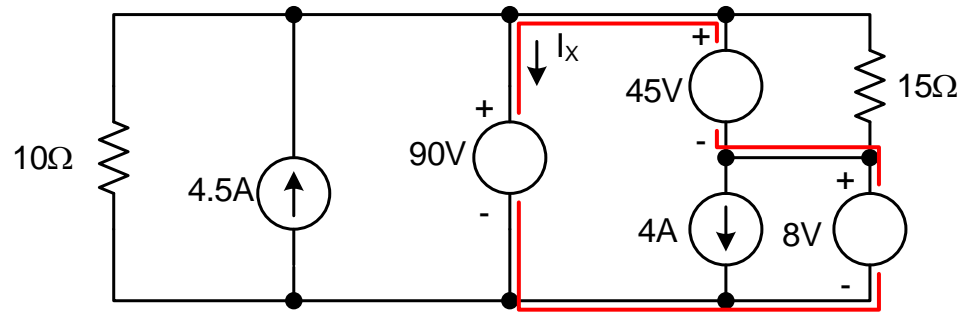

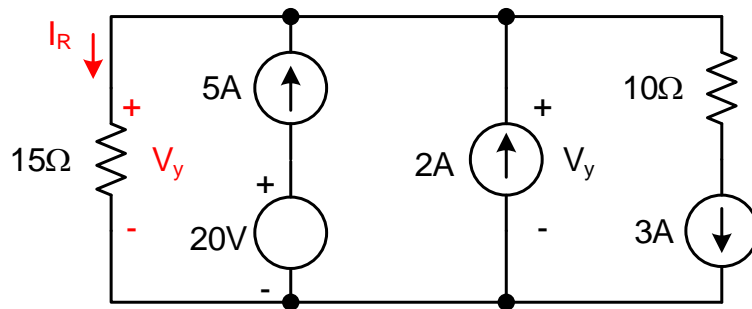
b. VALID. KCL: $I_R - 5 - 2 + 3 = 0$ $I_R = 4 \text{ A}$

Ohm and KVL: $V_y = (15\Omega)(4\text{A}) = 60\text{V}$



c. NOT VALID. KCL: $-3 + 2 - 0.5 \neq 0$

4. (25) Consider the network below.

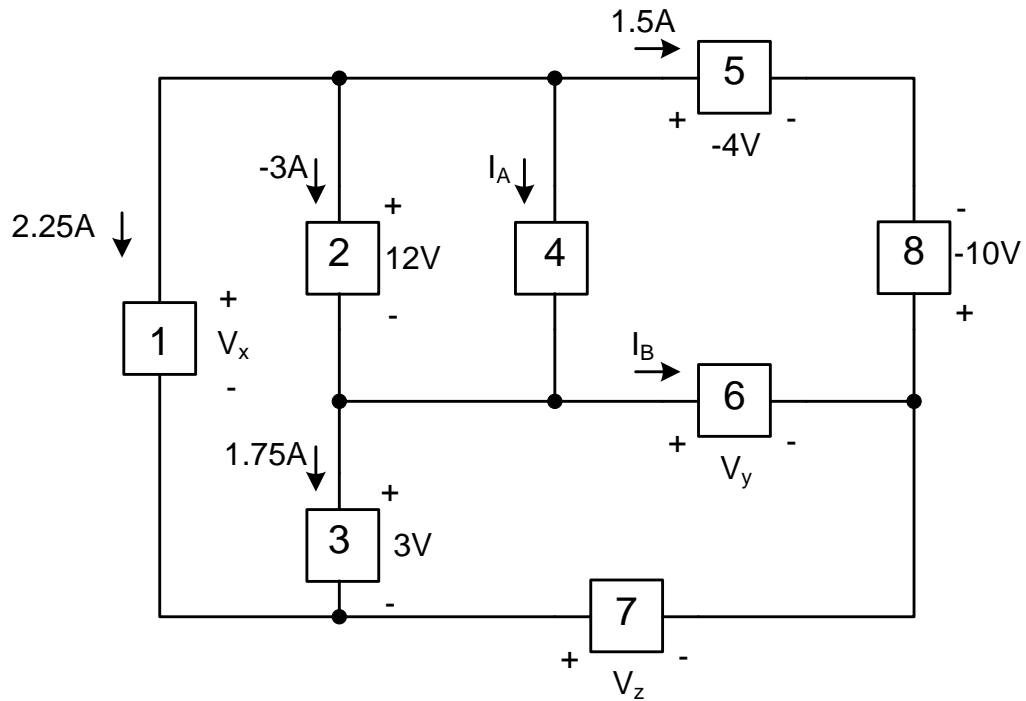

- Find I_A , I_B , V_x , V_y , and V_z .
- Find the power for each element in the circuit.
- Show that the total power developed is equal to the total power dissipated.

Solution.

- KCL:** $2.25A - 3A + 1.5A + I_A = 0$ $I_A = -0.75A$

KCL: $3A + 1.75A - (-0.75A) + I_B = 0$ $I_B = -5.5A$

KVL: $-V_x + 12V + 3V = 0$ $V_x = 15V$

KVL: $-12V + (-4V) - (-10V) - V_y = 0$ $V_y = -6V$

KVL: $-3V + (-6V) - V_z = 0$ $V_z = -9V$
- $P_1 = (2.25A)(15V) = 33.75W$

$P_2 = (-3A)(12V) = -36W$

$P_3 = (1.75A)(3V) = 5.25W$

$P_4 = (-0.75A)(12V) = -9W$

$P_5 = (1.5A)(-4V) = -6W$

$P_6 = (-5.5A)(-6V) = 33W$

$P_7 = (4A)(-9V) = -36W$

$$P_8 = -(1.5A)(-10V) = 15W$$

c. Total power developed = 87W

Total power dissipated = 87W