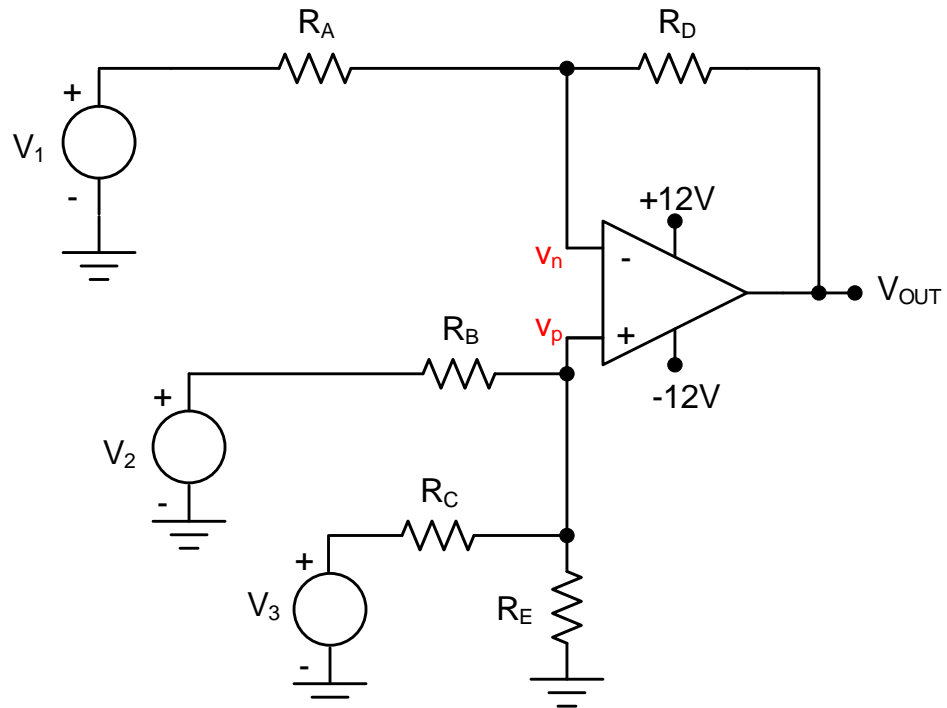


Homework Assignment 4 SOLUTION  
Due: Friday, Oct. 4, 2019

1. (20) Consider the op amp circuit shown below. Assume the op amp is ideal.



- a. Assuming linear operation, find an expression for  $V_{OUT}$  in terms of  $V_1$ ,  $V_2$ , and  $V_3$ .

**Solution.** The voltage  $v_p$  at the non-inverting input may be found using the node voltage method.

$$\frac{v_p - V_2}{R_B} + \frac{v_p - V_3}{R_C} + \frac{v_p}{R_E} = 0$$

$$v_p = \frac{\frac{V_2}{R_B} + \frac{V_3}{R_C}}{\frac{1}{R_B} + \frac{1}{R_C} + \frac{1}{R_E}}$$

Using KCL at the inverting input of the op amp we obtain

$$\frac{v_n - V_1}{R_A} + \frac{v_n - V_{OUT}}{R_D} = 0$$

Using the virtual short concept,  $v_p = v_n$ , we can combine these equations to obtain

$$V_{OUT} = -\frac{R_D}{R_A} V_1 + \left(1 + \frac{R_D}{R_A}\right) \frac{\frac{V_2}{R_B} + \frac{V_3}{R_C}}{\frac{1}{R_B} + \frac{1}{R_C} + \frac{1}{R_E}}$$

- b. Using this result, choose resistors so that

$$V_{OUT} = -5V_1 + 2.4V_2 + 1.2V_3.$$

Use standard resistors with 5% tolerances. The nominal coefficients (before taking into account tolerances) should all be within 10% of the desired coefficients.

**Solution.** The condition to achieve the desired coefficient for  $V_1$  is

$$\frac{R_D}{R_A} = 5.$$

We can choose  $R_D = 10k\Omega$  and  $R_A = 2k\Omega$ . As a consequence

$$\left(1 + \frac{R_D}{R_A}\right) = 6.$$

Therefore to achieve the desired coefficients for  $V_2$  and  $V_3$

$$\frac{\frac{1}{R_B}}{\frac{1}{R_B} + \frac{1}{R_C} + \frac{1}{R_E}} = \frac{2.4}{6} = 0.4$$

$$\frac{\frac{1}{R_C}}{\frac{1}{R_B} + \frac{1}{R_C} + \frac{1}{R_E}} = \frac{1.2}{6} = 0.2$$

Therefore

$$\frac{R_C}{R_B} = \frac{0.4}{0.2} = 2$$

We can choose  $R_C = 20k\Omega$  and  $R_B = 10k\Omega$ . With this choice

$$\frac{\frac{1}{20k\Omega}}{\frac{1}{10k\Omega} + \frac{1}{20k\Omega} + \frac{1}{R_E}} = 0.2$$


$$R_E = \left( \frac{1}{(0.2)20k\Omega} - \frac{1}{10k\Omega} - \frac{1}{20k\Omega} \right)^{-1} = 10k\Omega$$

**These choices are not unique, but the ratios must be maintained as follows:**

$$R_D:R_A = 5:1$$

$$R_C:R_B:R_E = 2:1:1$$

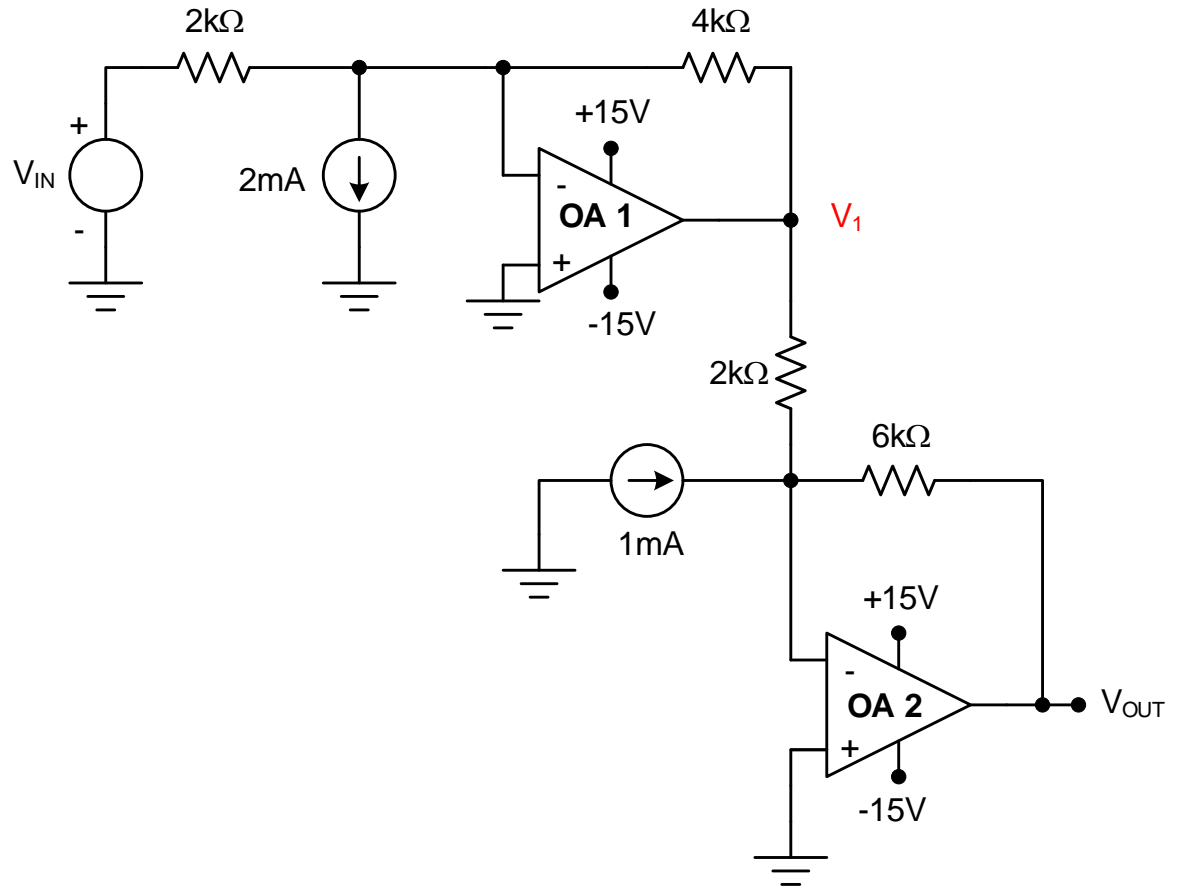2. (20) Consider the system of cascaded op amps shown below. Assume that the op amps are ideal.



- a. Find the range of  $V_{IN}$  for linear operation of OA1.

**Solution. For linear operation of OA1 the virtual short applies.**

$$\frac{0 - V_{IN}}{2k\Omega} + \frac{0 - V_1}{4k\Omega} + 2mA = 0$$

$$V_1 = 8V - 2V_{IN}$$

**For positive saturation,**

$$+15V = 8V - 2V_{IN}$$

**and**

$$V_{IN} = -3.5V.$$

**For negative saturation,**

$$-15V = 8V - 2V_{IN}$$

**and**

$$V_{IN} = +11.5V.$$

**For linear operation of OA1,**

$$-3.5V < V_{IN} < 11.5V.$$

- b. Find the range of  $V_{IN}$  for linear operation of OA2.

**Solution. For linear operation of OA2 the virtual short applies.**

$$\frac{0 - V_1}{2k\Omega} + \frac{0 - V_{OUT}}{6k\Omega} - 1mA = 0$$

$$V_{OUT} = -3V_1 - 6V = -30V + 6V_{IN}$$

**For positive saturation,**

$$+15V = -30V + 6V_{IN}$$

**and**

$$V_{IN} = 7.5V.$$

**For negative saturation,**

$$-15V = -30V + 6V_{IN}$$


**and**

$$V_{IN} = 2.5V.$$

**For linear operation of OA2,**

$$2.5V < V_{IN} < 7.5V.$$

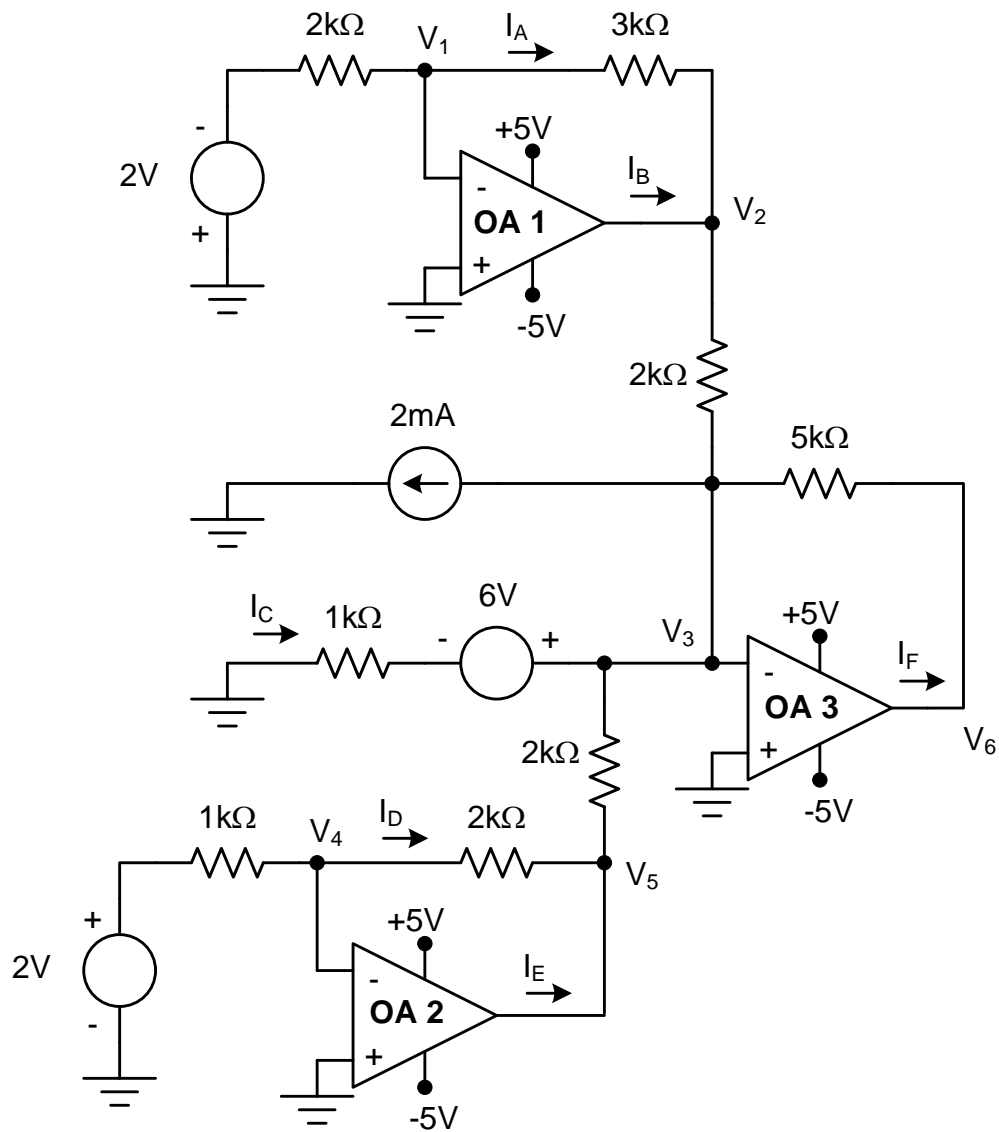3. (20) Find  $I_A$ ,  $I_B$ ,  $I_C$ ,  $I_D$ ,  $I_E$ ,  $I_F$ ,  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$ ,  $V_5$ , and  $V_6$ . Assume that the op amps are ideal.



**Solution.** We will start by assuming linear operation of OA1.

$$\frac{0 + 2V}{2k\Omega} + \frac{0 - V_2}{3k\Omega} = 0$$

$$V_2 = 3V$$

**Therefore OA1 is linear and**

$$V_1 = 0 \quad I_A = \frac{-2V}{2k\Omega} = -1mA$$

**We will next assume that OA2 is linear.**

$$\frac{0 - 2V}{1k\Omega} + \frac{0 - V_5}{2k\Omega} = 0$$

$$V_2 = -4V$$

**Therefore OA2 is linear and**

$$V_4 = 0 \quad I_D = \frac{2V}{1k\Omega} = 2mA$$

**We will next assume that OA3 is linear.**

$$\frac{0 - 3V}{2k\Omega} + 2mA + \frac{0 - 6V}{1k\Omega} + \frac{0 - (-4V)}{2k\Omega} + \frac{0 - V_6}{5k\Omega} = 0$$

$$V_6 = -17.5V$$

**Therefore OA3 is saturated.**

$$V_6 = -5V$$

$$\frac{V_3 - 3V}{2k\Omega} + 2mA + \frac{V_3 - 6V}{1k\Omega} + \frac{V_3 - (-4V)}{2k\Omega} + \frac{V_3 - (-5V)}{5k\Omega} = 0$$

$$5V_3 - 15V + 20V + 10V_3 - 60V + 5V_3 + 20V + 2V_3 + 10V = 0$$

$$V_3 = 1.136V$$


$$I_C = \frac{6V - 1.136V}{1k\Omega} = 4.864mA$$

$$I_F = \frac{-5V - 1.136V}{5k\Omega} = -1.227mA$$

$$I_B = \frac{3V - 0}{3k\Omega} + \frac{3V - 1.136V}{2k\Omega} = 1.932mA$$

$$I_E = \frac{-4V - 1.136V}{2k\Omega} + \frac{-4V - 0}{2k\Omega} = -4.568mA$$

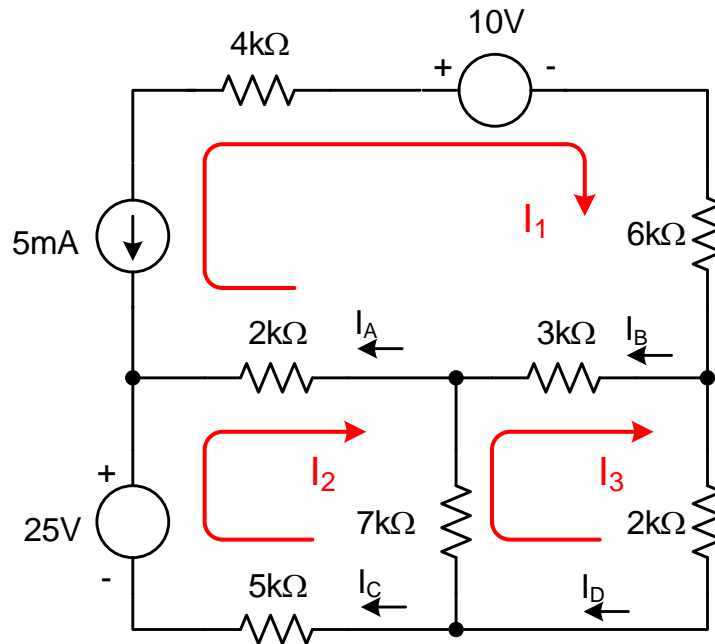4. (20) Determine  $I_A$ ,  $I_B$ ,  $I_C$ ,  $I_D$ , and the power for the 25V source.



**Solution. MCM using V, kΩ, and mA:**

1.  $I_1 = -5mA$  (known mesh current)

2.  $-25 + 2(I_2 + 5) + 7(I_2 - I_3) + 5I_2 = 0$

3.  $7(I_3 - I_2) + 3(I_3 + 5) + 2I_3 = 0$

$$\begin{bmatrix} 14 & -7 \\ -7 & 12 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 15 \\ -15 \end{bmatrix} \quad I_2 = 0.630 \text{ mA}$$

$$I_3 = -0.882 \text{ mA}$$

$$I_A = I_1 - I_2 = -5.63 \text{ mA}$$

$$I_B = I_1 - I_3 = -4.12 \text{ mA}$$


$$I_C = I_2 = 0.630 \text{ mA}$$

$$I_D = I_3 = -0.88 \text{ mA}$$

$$P_{25V} = -(25V)I_2 = -15.75mW$$



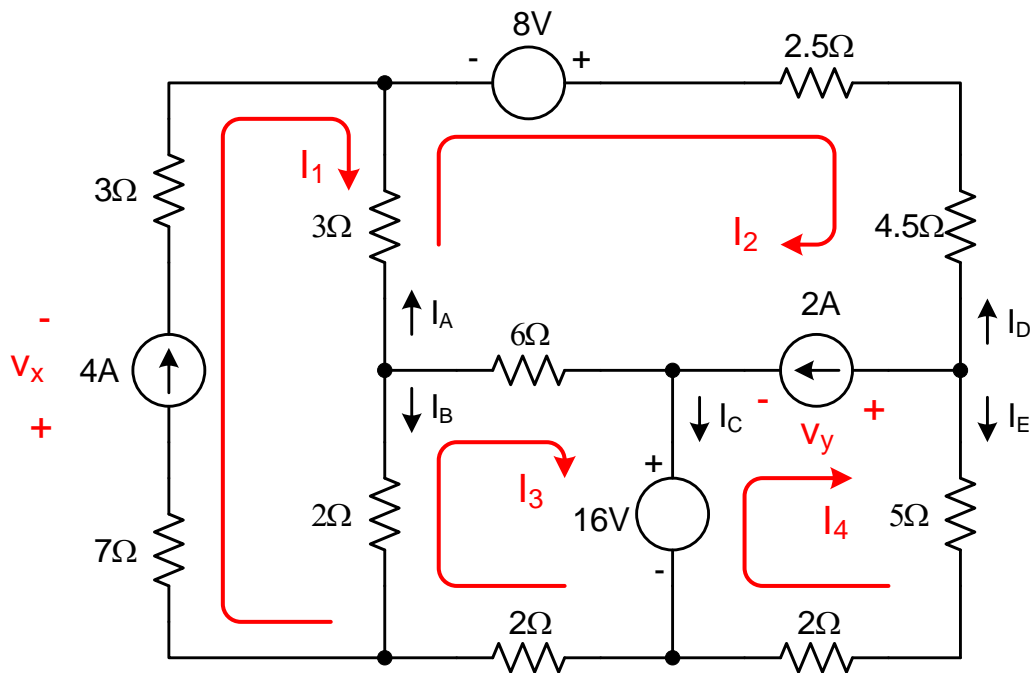5. (20) For the circuit shown, find  $I_A$ ,  $I_B$ ,  $I_C$ ,  $I_D$ ,  $I_E$ , and the power for each of the sources.



**Solution. MCM using V,  $\Omega$ , and A:**

1.  $I_1 = 4A$  (known mesh current)

3.  $2(I_3 - 4) + 6(I_3 - I_2) + 16 + 2I_3 = 0$

24.  $-8 + 7I_2 + 7I_4 - 16 + 6(I_2 - I_3) + 3(I_2 - 4) = 0$  (supermesh)

CS.  $I_2 - I_4 = 2$

24CS.  $-8 + 7I_2 + 7(I_2 - 2) - 16 + 6(I_2 - I_3) + 3(I_2 - 4) = 0$

$$\begin{bmatrix} 23 & -6 \\ -6 & 10 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ -8 \end{bmatrix}$$

$$I_2 = 2.33A$$

$$I_3 = 0.60A$$

$$I_4 = 0.33A$$

$$I_A = I_2 - I_1 = -1.67 A$$

$$I_B = I_1 - I_3 = 3.4 A$$

$$I_C = I_3 - I_4 = 0.27 A$$

$$I_D = -I_2 = -2.33 A$$

$$I_E = I_4 = 0.33A$$

$$v_x + 15I_1 - 3I_2 - 2I_3 = 0$$

$$v_x = -51.8V$$

$$P_{4A} = (-51.8)(4A) = -207W$$

$$-v_y + 7I_4 - 16 = 0$$

$$v_y = -13.69V$$

$$P_{2A} = (2A)v_y = -27.4W$$

$$P_{8V} = -(8V)(I_2) = -18.64W$$

$$P_{16V} = (16V)(I_3 - I_4) = 4.32W$$