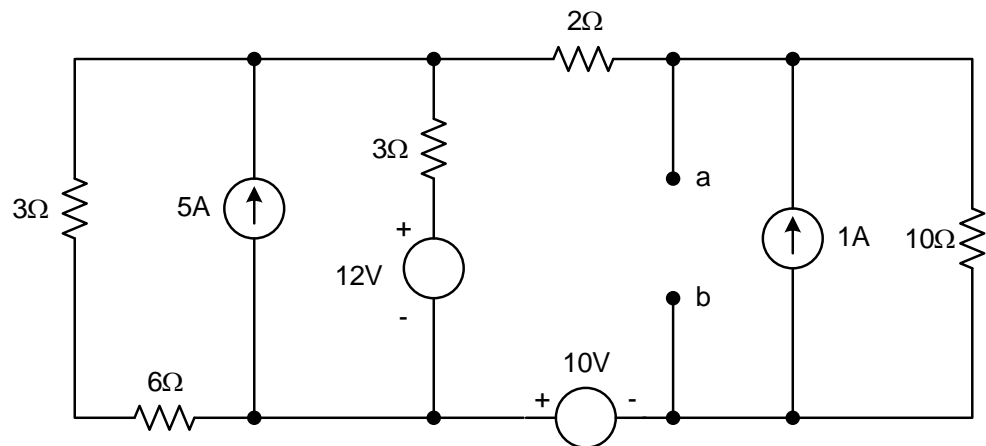


Homework Assignment 5 Solution
Due: Oct. 11, 2019


NOTE ON SIGNS: The open-circuit voltage V_{oc} is the open-circuit value of V_{ab} . The short-circuit current is the current which flows from a to b in a wire connected between these two terminals. Please use these conventions throughout this assignment.

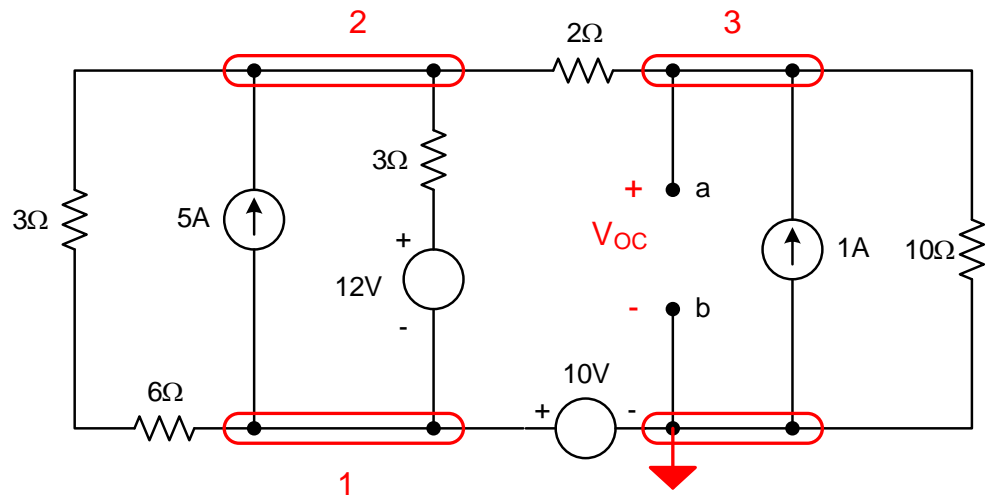1. (20) Find the Thevenin equivalent with respect to the terminals a and b in the circuit shown.



Solution.

Open-circuit analysis using the NVM with V, A, and Ω :



1. $V_1 = 10V$ (known node voltage)

$$2. \frac{V_2 - 10}{9} - 5 + \frac{V_2 - 12 - 10}{3} + \frac{V_2 - V_3}{2} = 0$$

$$3. \frac{V_3 - V_2}{2} - 1 + \frac{V_3}{10} = 0$$


$$2. 2V_2 - 20 - 90 + 6V_2 - 132 + 9V_2 - 9V_3 = 0$$

$$3. 5V_3 - 5V_2 - 10 + V_3 = 0$$

$$\begin{bmatrix} 17 & -9 \\ -5 & 6 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 242 \\ 10 \end{bmatrix} \quad V_2 = 27.05 V \quad V_3 = 24.21 V$$

$$V_{OC} = 24.21 V = V_{Th}$$

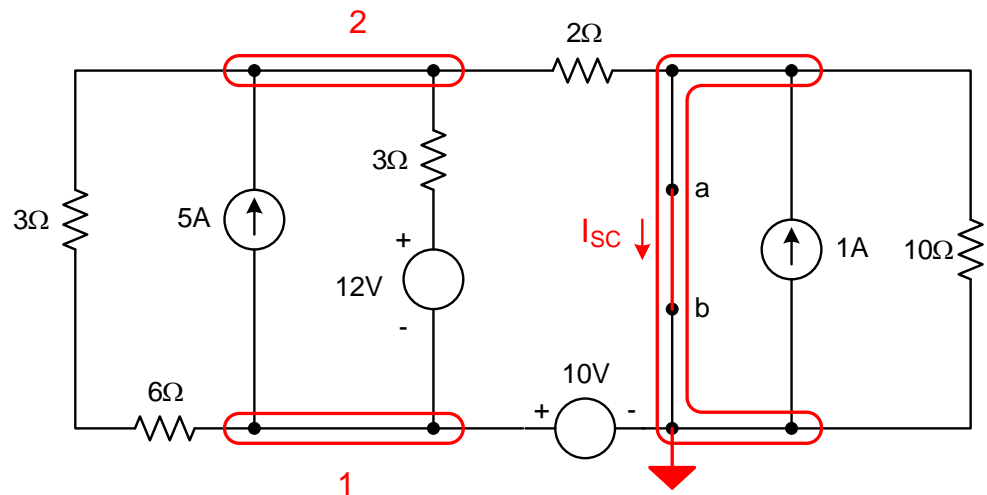Short-circuit analysis using the NVM with V, A, and Ω :



1. $V_1 = 10V$ (known node voltage)

$$2. \frac{V_2 - 10}{9} - 5 + \frac{V_2 - 12 - 10}{3} + \frac{V_2}{2} = 0$$

$$2. 2V_2 - 20 - 90 + 6V_2 - 132 + 9V_2 = 0$$


$$2. 17V_2 - 242 = 0$$

$$V_2 = 14.24 V$$

$$I_{SC} = \frac{V_2}{2\Omega} + 1A = 8.12 A$$


$$R_{Th} = \frac{V_{OC}}{I_{SC}} = \frac{24.21V}{8.12A} = 2.98\Omega$$

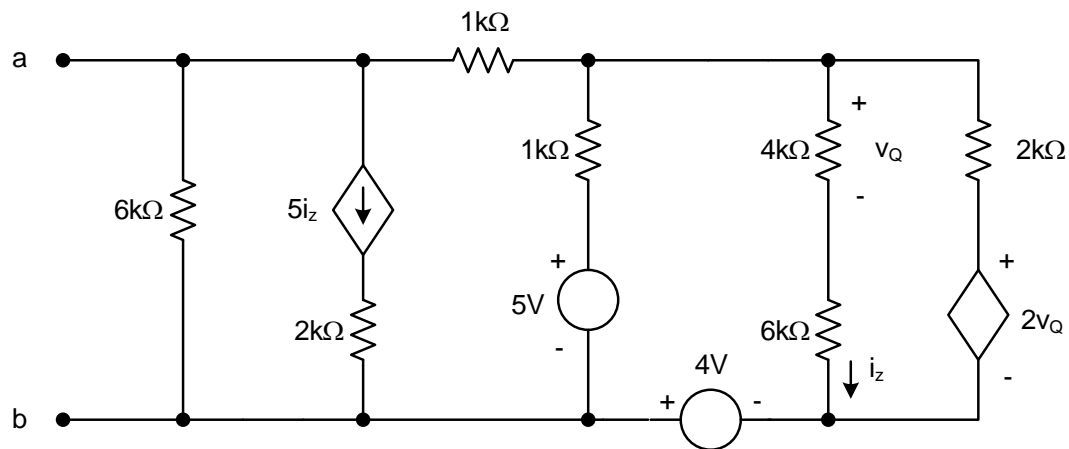2. (20) Determine the open-circuit voltage, the short-circuit current, the Thevenin equivalent, and the Norton equivalent with respect to the terminals a and b in the circuit shown.



Solution.

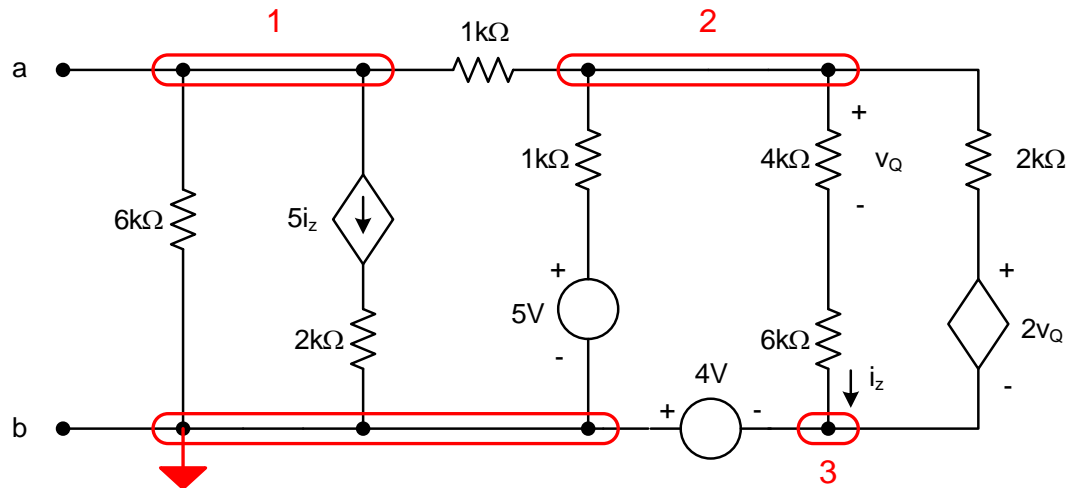Open-circuit analysis using the NVM with V, mA, and kΩ:



3. $V_3 = -4V$ (known node voltage)

$$1. \frac{V_1}{6} + 5i_z + \frac{V_1 - V_2}{1} = 0$$

$$2. \frac{V_2 - V_1}{1} + \frac{V_2 - 5}{1} + \frac{V_2 + 4}{10} + \frac{V_2 - 2v_Q + 4}{2} = 0$$

$$\text{CS. } i_z = \frac{V_2 + 4}{10}$$

$$\text{VS. } v_Q = \left(\frac{V_2 + 4}{10} \right) 4 = \frac{4V_2 + 16}{10}$$

$$1\text{CS. } \frac{V_1}{6} + \frac{V_2 + 4}{2} + \frac{V_1 - V_2}{1} = 0$$

$$2\text{VS. } \frac{V_2 - V_1}{1} + \frac{V_2 - 5}{1} + \frac{V_2 + 4}{10} + \frac{V_2 + 4}{2} - \frac{4V_2 + 16}{10} = 0$$


1CS. $V_1 + 3V_2 + 12 + 6V_1 - 6V_2 = 0$

2VS. $10V_2 - 10V_1 + 10V_2 - 50 + V_2 + 4 + 5V_2 + 20 - 4V_2 - 16 = 0$

$$\begin{bmatrix} 7 & -3 \\ -10 & 22 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -12 \\ 42 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -1.113V \\ 1.403V \end{bmatrix}$$

$V_{OC} = V_1 = -1.113V = V_{Th}$

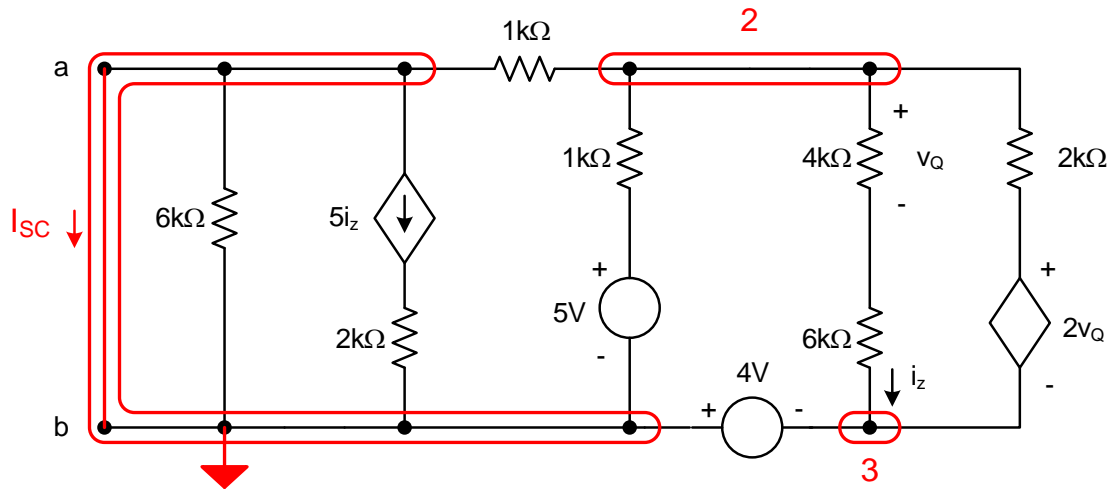Short-circuit analysis using the NVM with V, mA, and k Ω :



3. $V_3 = -4V$ (known node voltage)

2. $\frac{V_2}{1} + \frac{V_2-5}{1} + \frac{V_2+4}{10} + \frac{V_2-2v_Q+4}{2} = 0$

CS. $i_z = \frac{V_2+4}{10}$

VS. $v_Q = \left(\frac{V_2+4}{10}\right) 4 = \frac{4V_2+16}{10}$

2VS. $\frac{V_2}{1} + \frac{V_2-5}{1} + \frac{V_2+4}{10} + \frac{V_2+4}{2} - \frac{4V_2+16}{10} = 0$

2VS. $10V_2 + 10V_2 - 50 + V_2 + 4 + 5V_2 + 20 - 4V_2 - 16 = 0$


2VS. $22V_2 = 42$

$V_2 = 1.909V$

$I_{SC} = \frac{V_2}{1k\Omega} - 5i_z = \frac{V_2}{1k\Omega} - \frac{V_2+4V}{2k\Omega} = -1.046mA$


$R_{Th} = \frac{V_{OC}}{I_{SC}} = \frac{-1.113V}{-1.046mA} = 1.064k\Omega$

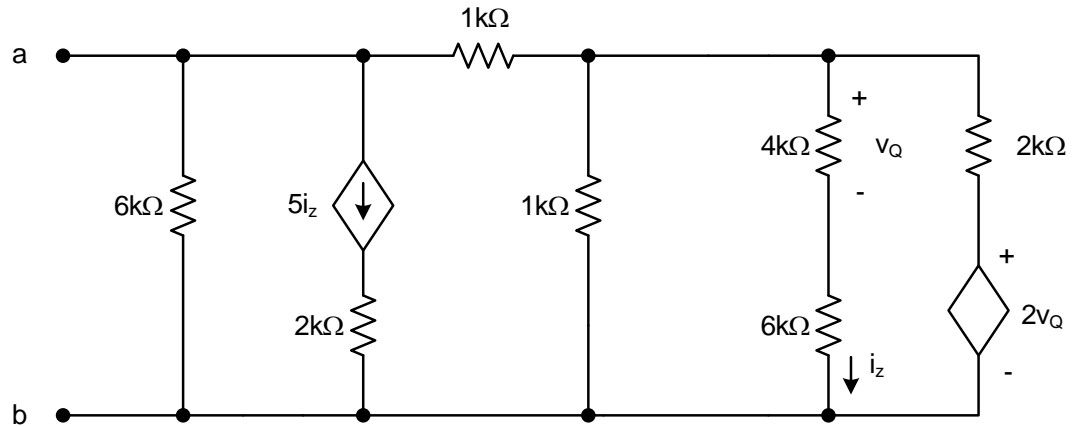3. (20) Determine the Thevenin resistance for the network shown below.



Solution.

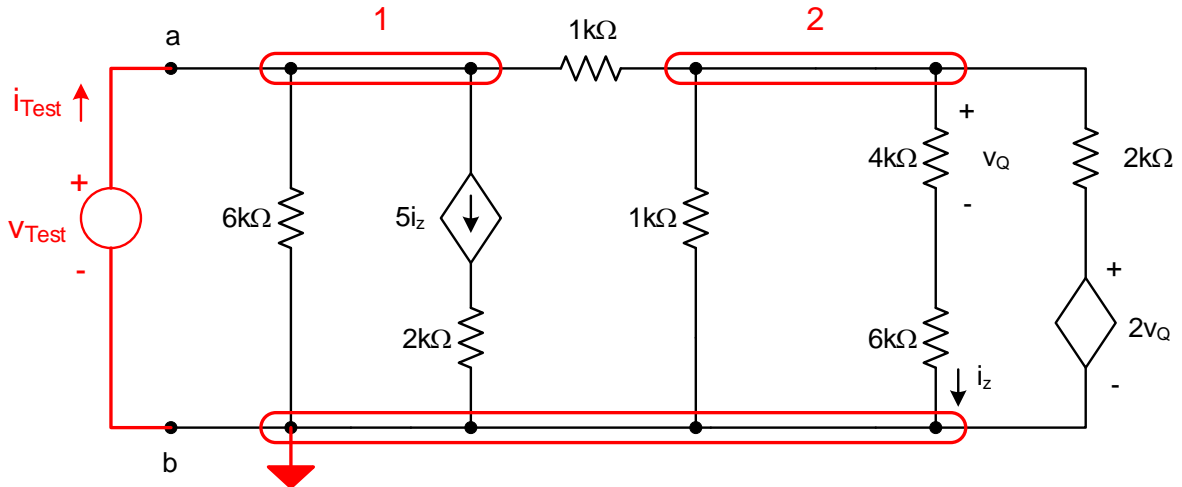Test-source analysis using the NVM with V, mA, and kΩ:



1. $V_1 = V_{Test}$ (known node voltage)

2. $\frac{V_2 - V_{Test}}{1} + \frac{V_2}{1} + \frac{V_2}{10} + \frac{V_2 - 2v_Q}{2} = 0$

CS. $i_z = \frac{V_2}{10}$

VS. $v_Q = \frac{4V_2}{10}$

2VS. $\frac{V_2 - V_{Test}}{1} + \frac{V_2}{1} + \frac{V_2}{10} + \frac{V_2}{2} - \frac{4V_2}{10} = 0$

2VS. $10V_2 - 10V_{Test} + 10V_2 + V_2 + 5V_2 - 4V_2 = 0$


2VS. $22V_2 = 10V_{Test}$

$V_2 = \left(\frac{10}{22}\right) V_{Test}$



$$I_{Test} = \frac{V_{Test}}{6k\Omega} + 5i_z + \frac{V_{Test} - V_2}{1k\Omega} = \frac{V_{Test}}{6k\Omega} + 5\left(\frac{10V_{Test}/22}{10k\Omega}\right) + \frac{V_{Test} - 10V_{Test}/22}{1k\Omega}$$




$$R_{Th} = \frac{V_{Test}}{I_{Test}} = \left[\frac{1}{6k\Omega} + \frac{50/22}{10k\Omega} + \frac{1}{1k\Omega} - \frac{10/22}{1k\Omega} \right]^{-1} = 1.0645k\Omega$$



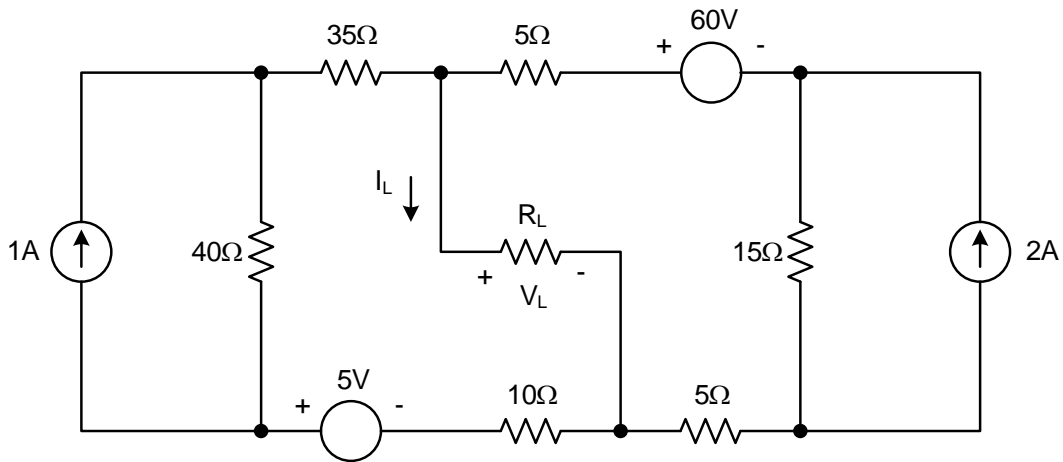
4. (20) For the network shown below, plot I_L as a function of R_L , plot V_L as a function of R_L , and plot P_L as a function of R_L . Use a range of R_L from $R_{Th}/4$ to $4R_{Th}$.



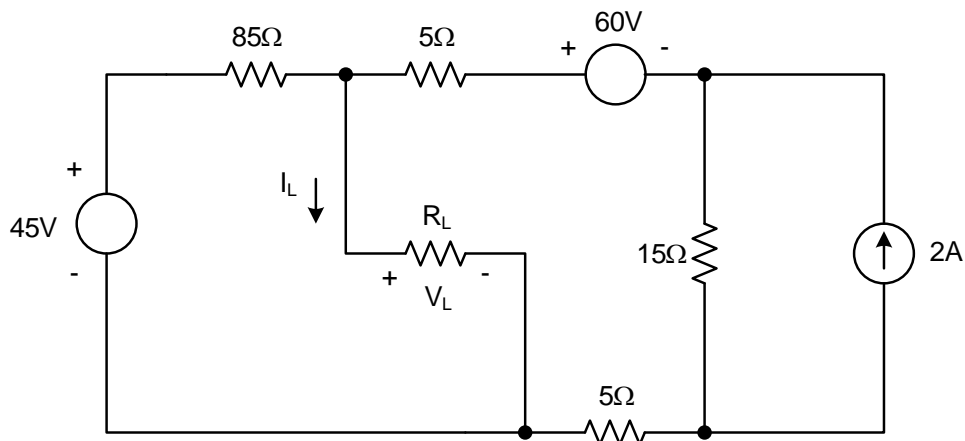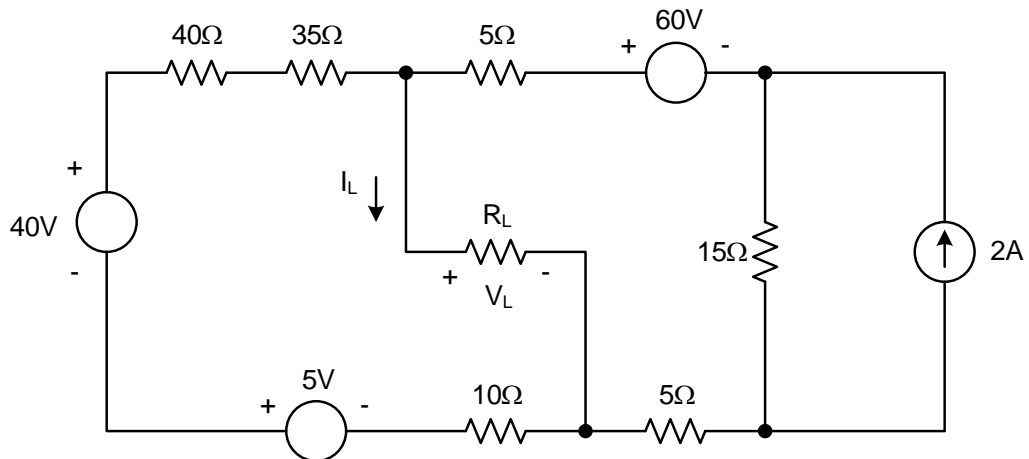Solution. Source transformations may be used in conjunction with simplifications.



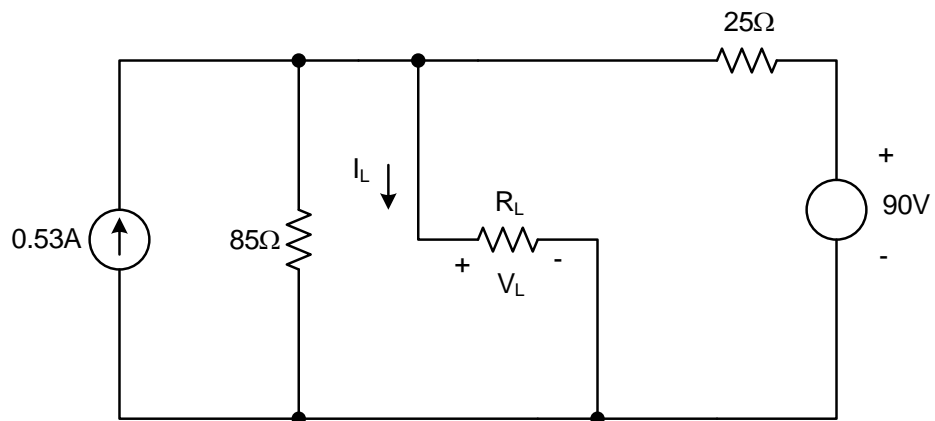
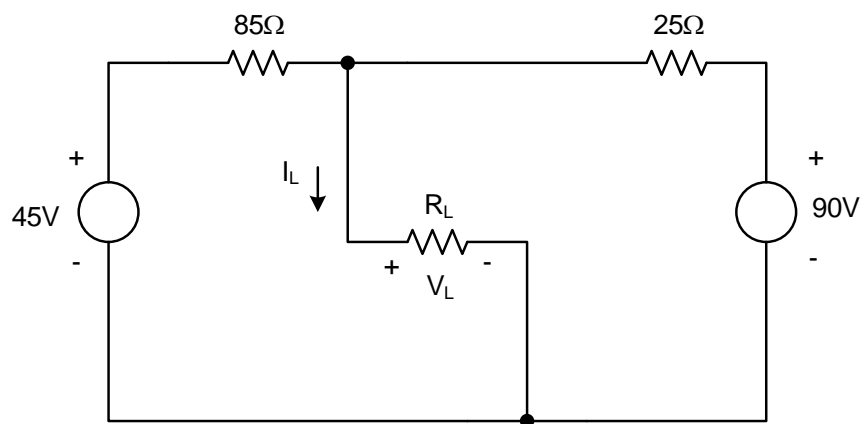
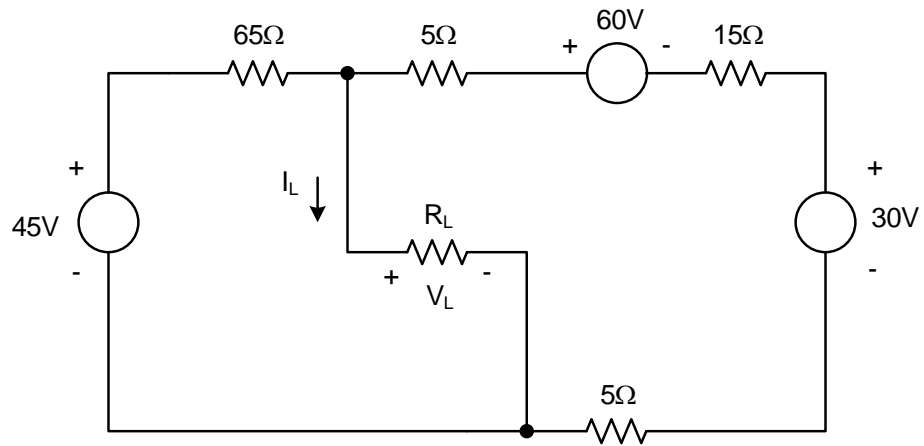


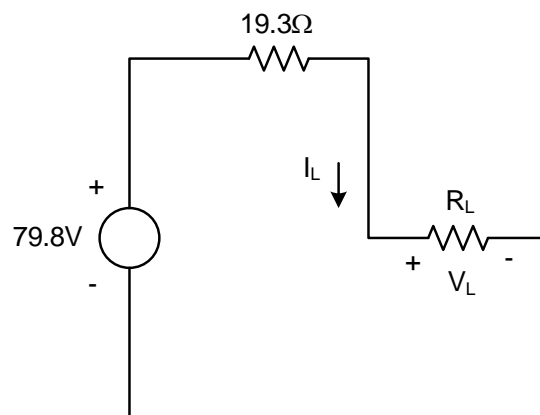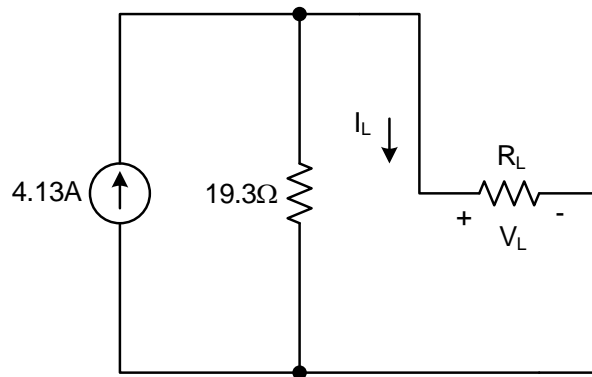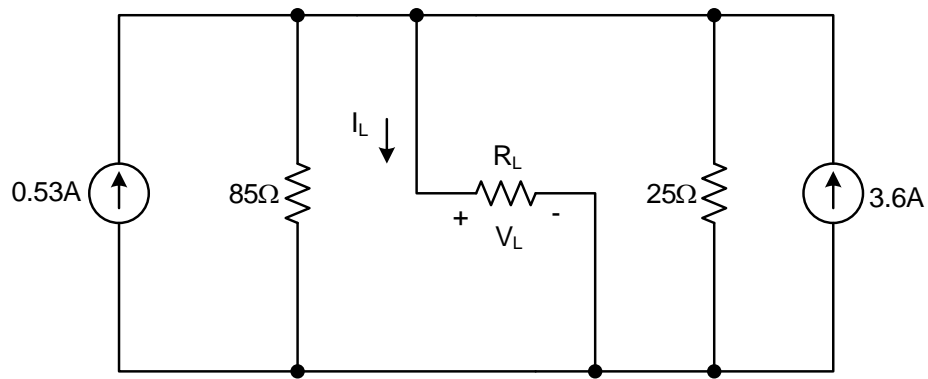


$$I_L = \frac{79.8V}{19.3\Omega + R_L}$$

$$V_L = \left(\frac{79.8V}{19.3\Omega + R_L} \right) R_L$$
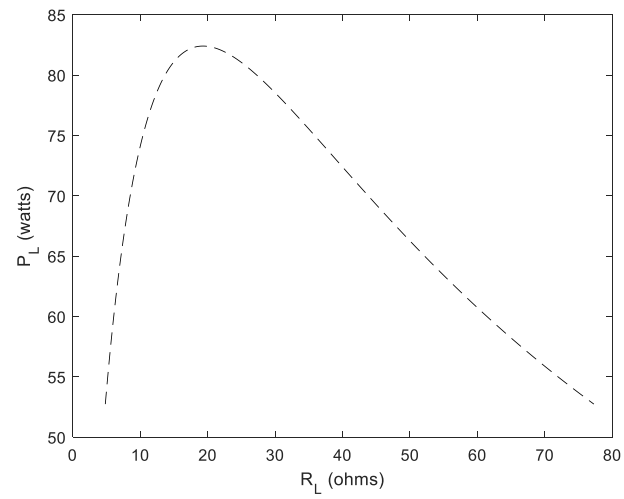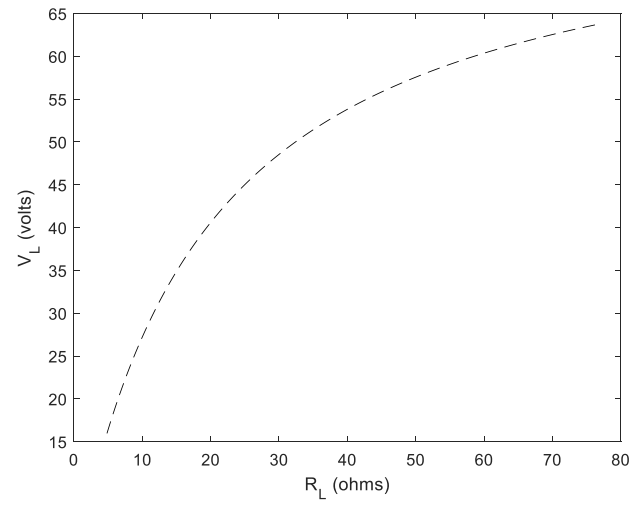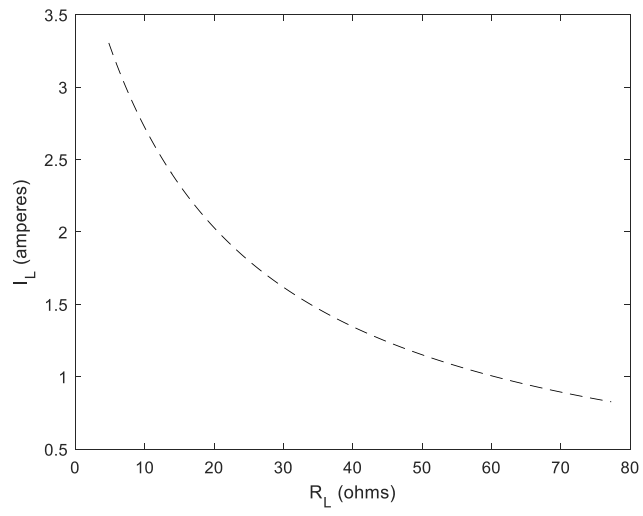
$$P_L = I_L V_L = \left(\frac{79.8V}{19.3\Omega + R_L} \right)^2 R_L$$



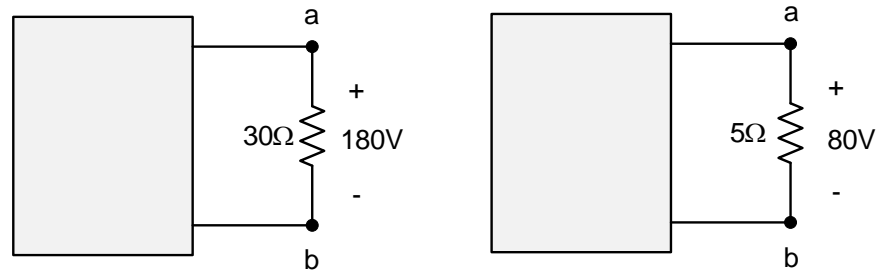5. (20) The figures below represent two measurements made using two different load resistances connected to the same two-terminal network contained within an enclosure. The network in the enclosure is a linear network involving resistances, independent sources, and dependent sources.
- (a) Find the open-circuit voltage for the network contained in the box.
- (b) Find the value of the resistance R_L which will dissipate maximum power.



Solution.

Test 1. $180V = V_{Th} \left(\frac{30\Omega}{R_{Th} + 30\Omega} \right)$

Test 2. $80V = V_{Th} \left(\frac{5\Omega}{R_{Th} + 5\Omega} \right)$

Test 1. $(180V)R_{Th} + (180V)(30\Omega) = V_{Th}(30\Omega)$

Test 2. $(80V)R_{Th} + (80V)(5\Omega) = V_{Th}(5\Omega)$

Test 2. $(180V)R_{Th} + (900V\Omega) = V_{Th}(11.25\Omega)$

Subtracting Test 2 from Test 1: $(4500V\Omega) = V_{Th}(18.75\Omega)$

$V_{Th} = 240V$

Test 1. $(180V)R_{Th} + (180V)(30\Omega) = 240V(30\Omega)$

$R_{Th} = 10\Omega$

a. The open-circuit voltage is $V_{OC} = 240V$.

b. The load resistance which will dissipate maximum power is $R_L = 10\Omega$.

