
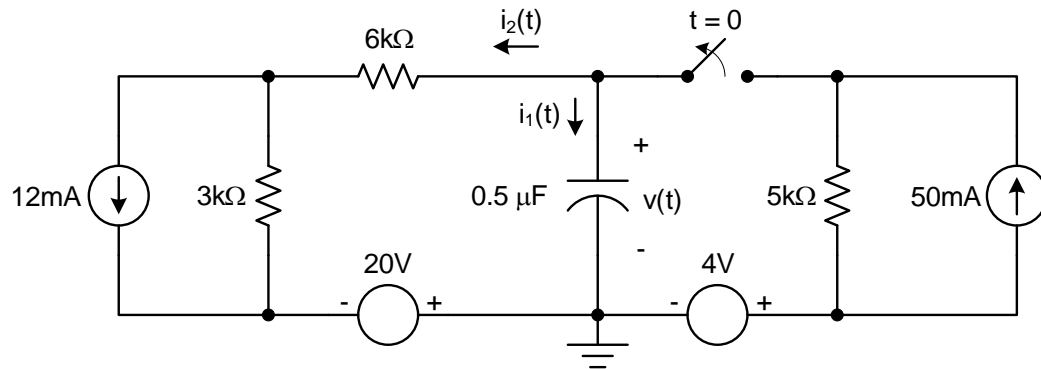


Homework Assignment 6  
Due: October 25, 2019

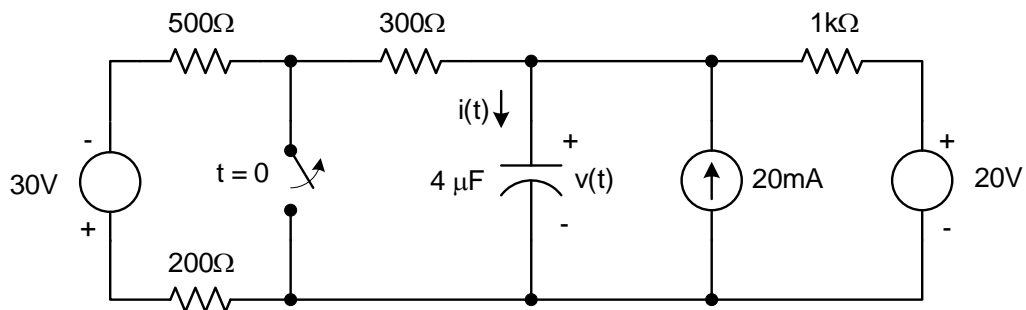
1. The switch has been closed for a long time before opening at  $t = 0$ . Find  $v(t)$ ,  $i_1(t)$ , and  $i_2(t)$  for  $t \geq 0^+$ .




2. The switch has been closed a long time before opening at  $t = 0$ . Find the initial and final energy stored in the capacitor. Determine  $i(t)$  and  $v(t)$  for  $t \geq 0^+$ .



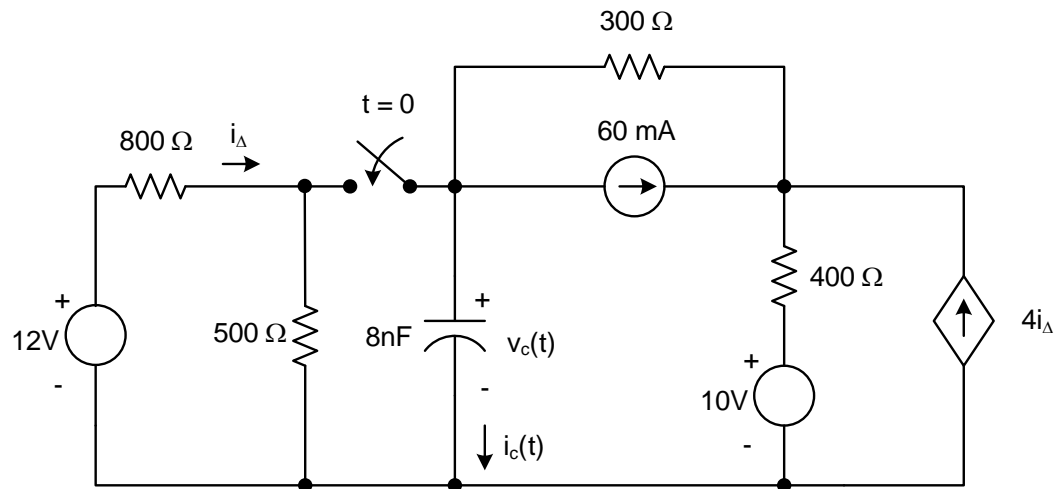3. The switch has been open a long time before closing at  $t = 0$ . Determine  $i_c(t)$  and  $v_c(t)$  for  $t \geq 0^+$ .



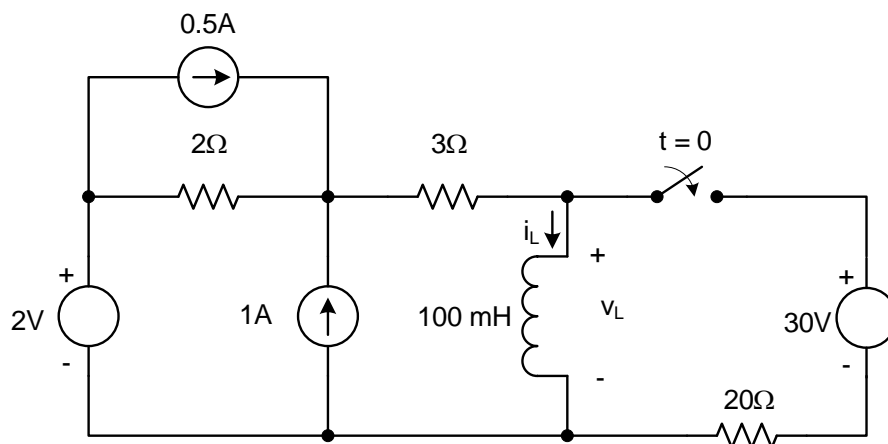4. The switch has been open for a long time before closing at  $t = 0$ . Find  $i_L(t)$  and  $v_L(t)$  for  $t \geq 0^+$ . Find the initial and final energy stored in the inductor.



5. In the circuit below, the make-before-break switch has been in position “a” for a long time before being switched to position “b” at  $t = 0$ . Find  $v_R(t)$ ,  $i_1(t)$ , and  $i_2(t)$  for  $t \geq 0^+$ . Find the initial and final energy for each inductor.

