

Electrical Circuits: Homework #1



Due on September 9, 2019 at 9:00am

Professor J.E.Ayers

Patrik Sokolowski

Problem 1

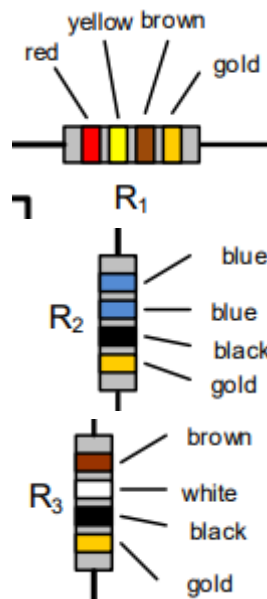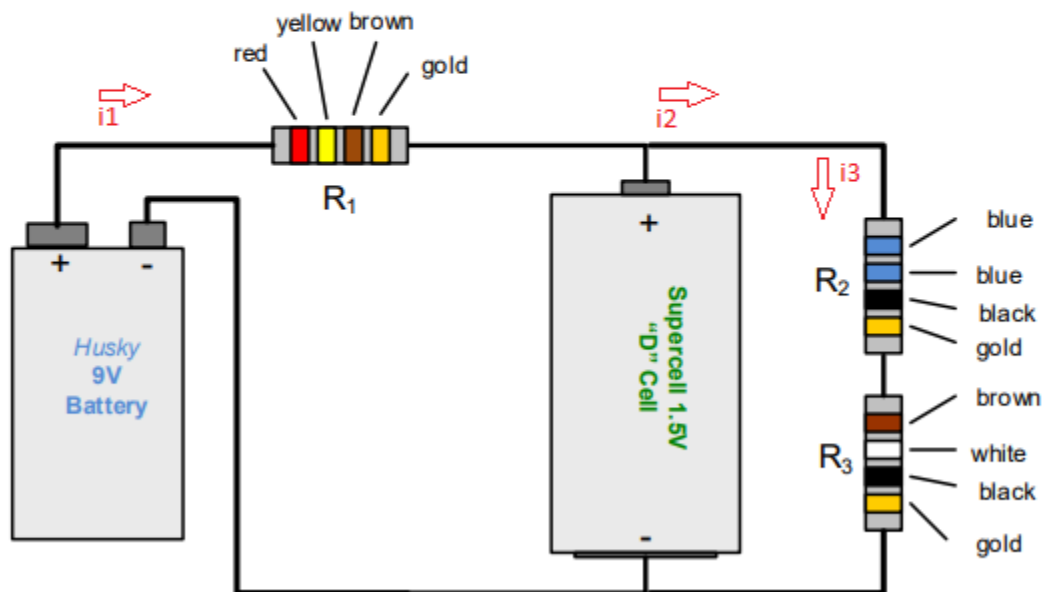1. Two batteries and three resistors are connected as shown below. a) Does conventional current enter or leave the positive terminal of the 9 V battery? b) Do electrons enter or leave the positive terminal of the 9 V battery? c) Does the 9 V battery develop or dissipate power? d) Does conventional current enter or leave the positive terminal of the 1.5 V battery? e) What is the power for the 1.5 V battery? (Use the passive sign convention.) f) Find the power for each of the resistors.



Red (2) Yellow (4) Brown ($\cdot 10^1$) = 250Ω

Blue (6) Blue (6) Black ($\cdot 10^0$) = 66Ω

Brown (1) White (9) Black ($\cdot 10^0$) = 19Ω

- A) Conventional current leaves the terminal of the 9V battery.
- B) Electrons enter the terminal of the 9V battery.
- C) Power is developed from the 9V battery (negative, leaving battery).
- D) Conventional current enters the 1.5V battery.
- E) $p = 1.5V \cdot I_2 = 1.5V \cdot 13.65 = 20.475mW$

$$I_2 = I_1 - I_3 = 31.25 - 17.6 = 13.65mA.$$

$$I_1 = \frac{9-1.5}{R_1} = \frac{9-1.5}{240} = 31.25mA.$$

$$I_3 = \frac{1.5}{R_2+R_3} = \frac{1.5}{85} = 17.6mA.$$

F) Power in resistors:


$$p \text{ in } R_1 = (I_1)^2 \cdot R_1 = (31.25 \cdot 10^{-3})^2 \cdot (240) = 234.4mW$$

$$p \text{ in } R_2 = (I_3)^2 \cdot R_2 = (17.6 \cdot 10^{-3})^2 \cdot (66) = 20.44mW$$

$$p \text{ in } R_3 = (I_3)^2 \cdot R_3 = (17.6 \cdot 10^{-3})^2 \cdot (19) = 5.89mW$$

Problem 2

2. Consider the resistive circuit below.

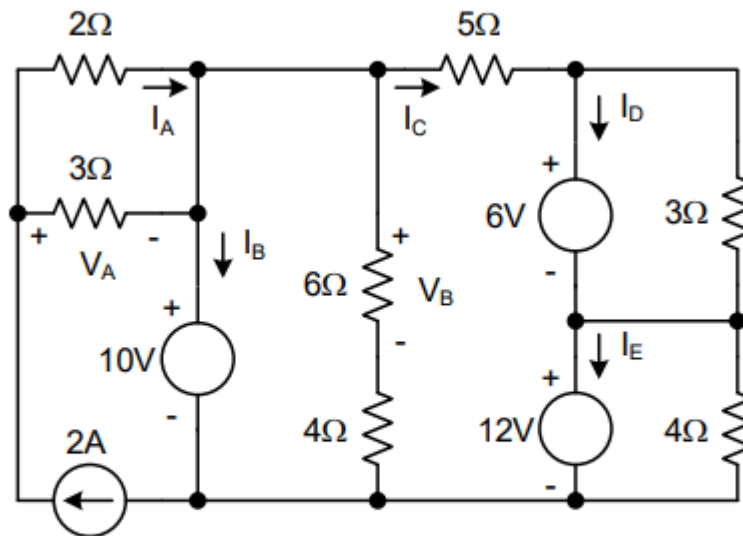

- Find V_A , V_B , I_A , I_B , I_C , I_D , and I_E .
- Find the power for each of the sources, using the passive sign convention. Do any of the sources *dissipate* power?

A) Values:

$$V_A = 2(1.2) = 2.4V$$

$$V_B = 6(I_E) = 6(1) = 6V$$

$$I_A = \frac{3}{2+3} \cdot 2 = 1.2A$$

$$I_B = 2 - (-16) - 1 = 2.6A$$

$$I_C = -\frac{10-18}{5} = -1.6A$$

$$I_D = (KCL)I_C = I_D + 2A, I_D = -2 - 1.6 = -3.6A$$

$$I_E = (KCL)2 + I_D = I_E + 3, I_E = 2 - 3 - 3.6 = -4.6A$$

B) Values:

$$\text{power } 2A = (2)(-12.4) = -24.8W$$

$$\text{power } 10V = (10)(I_B) = 10 \cdot \frac{13}{5} = 26W (\text{Dissipated})$$

$$\text{power } 6V = (6)(I_E) = 6\left(\frac{-18}{5}\right) = -21.6W$$

$$\text{power } 12V = (12)(I_E) = 12(-4.6) = -55.2W$$




Problem 3

3. Consider the following three circuits.

(a) Is circuit a valid? If it is, find I_x . If not, show a violation of Kirchhoff's laws.

(b) Is circuit b valid? If so, determine V_y . If not, show a violation of Kirchhoff's laws.

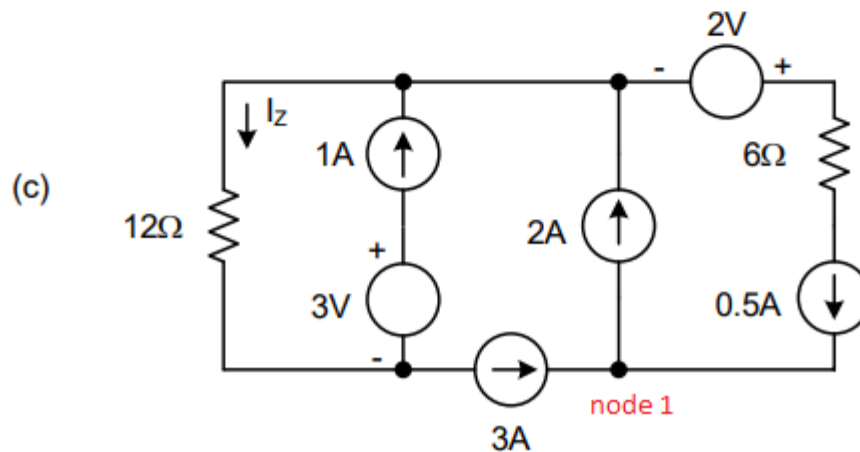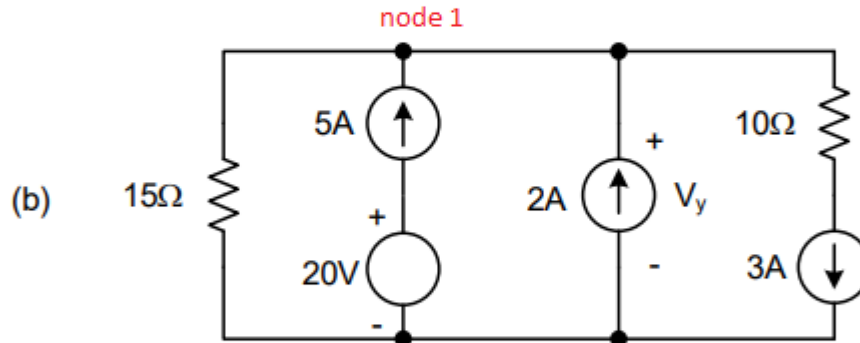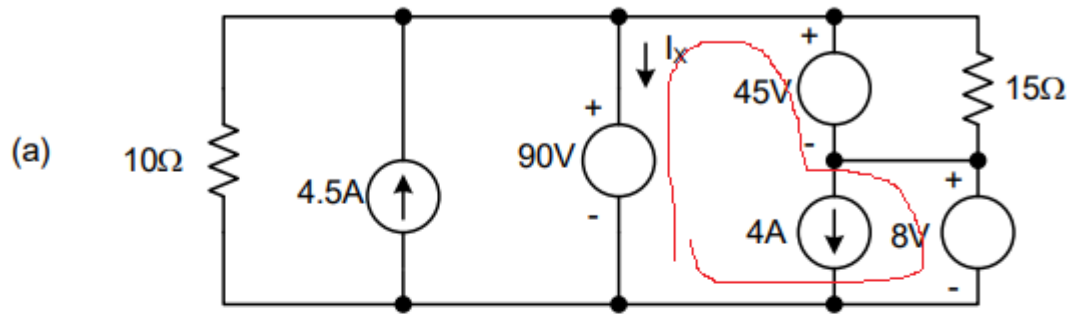(c) Is circuit c valid? If so, find I_z . If not, show a violation of Kirchhoff's laws.




A) using KVL: $-90 + 45 + 8 = 0$, $-37 \neq 0$. Invalid Circuit.

B) using KCL (node 1): $(V_y/15) - 5 - 2 + 3 = 0$, $V_y = 20V$, $\frac{20}{15} - 5 - 2 + 3 = 0$, $-2.67 \neq 0$. Invalid Circuit.

C) using KCL (node 1): $3 + 0.5 = 2A$, $3.5 \neq 2$. Invalid Circuit.

Problem 4

4. Consider the network below.

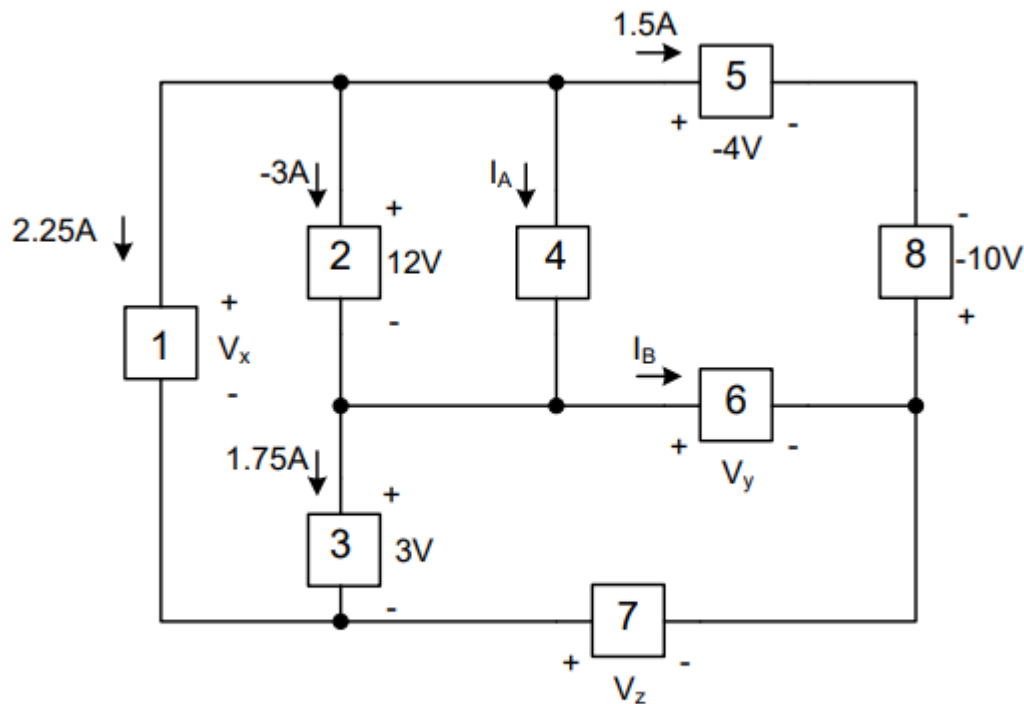

- Find I_A , I_B , V_x , V_y , and V_z .
- Find the power for each element in the circuit.
- Show that the total power developed is equal to the total power dissipated.

A) Values:

$$V_x = (KVL) - V_x + 12 + 3 = 0, = 15V$$

$$V_y = (KVL) - 12 - 4 + 10 - V_y = 0, = -6V$$

$$V_z = (KVL) - 3 + V_y - V_z = 0, V_z = -3 + V_y = -3 - 6 = 9V$$

$$I_A = (KCL) I_A + 2.25 - 3 + 1.5 = 0, I_A = -0.75A$$

$$I_B = (KCL) I_B = -3 - 0.75 - 0.75 = -5.5A$$

B) Values:

$$p = vi$$

$$1: (15V)(2.25) = 33.75W$$

$$2: (12V)(-3) = -36W$$

$$3: (3V)(1.75) = 5.25W$$

$$4: (12V)(-0.75) = -9W$$

$$5: (-4V)(1.5) = -6W$$

$$6: (-6V)(-5.5) = 33W$$

$$7: (-4V)(9) = -36W$$

$$8: (10V)(1.5) = 15W$$

C) $33.75 - 36 + 5.25 - 9 - 6 + 33 - 36 + 15 = 0$
= 0 , so total power developed = total power dissipated.