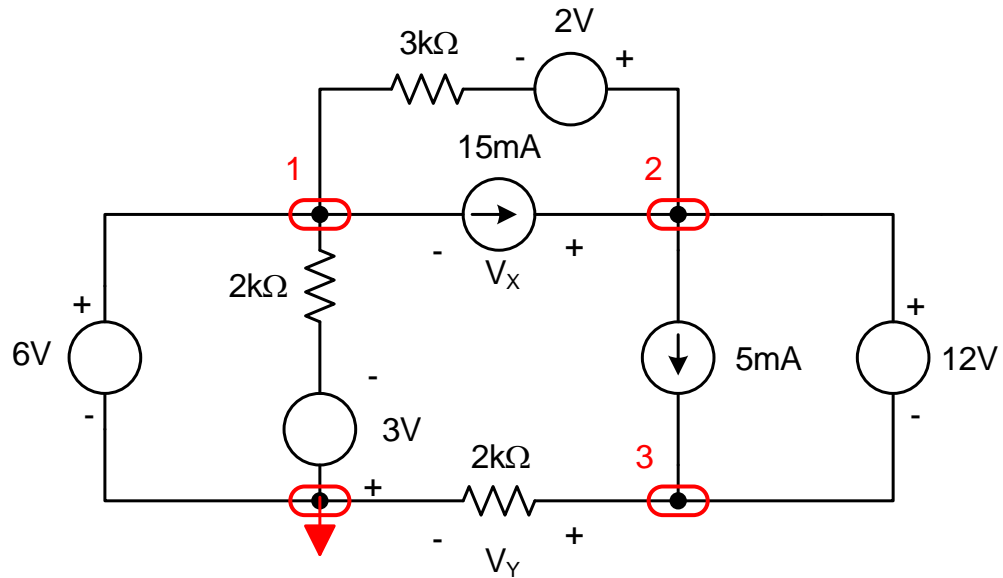


Homework Assignment 3 **SOLUTION**
Due: Friday, Sept. 20, 2019

1. (20) For the network below find, V_X , V_Y , and the power in the 15 mA source.



Solution. Node voltage method using V, kΩ, and mA.

1. $V_1 = 6V$ (known node voltage)

23. $-15 + \frac{V_2 - 2 - 6}{3} + \frac{V_3}{2} = 0$ (supernode)

VS. $V_3 = V_2 - 12$ (voltage source)

23VS. $-15 + \frac{V_2 - 8}{3} + \frac{V_2 - 12}{2} = 0$

23VS. $-90 + 2V_2 - 16 + 3V_2 - 36 = 0$

$5V_2 - 142 = 0 \quad V_2 = 28.4V$


$V_3 = V_2 - 12V = 16.4V$

$V_X = V_2 - V_1 = 22.4V$


$V_Y = V_3 = 16.4V$

$P_{15mA} = (15mA)(V_1 - V_2) = -336mW$

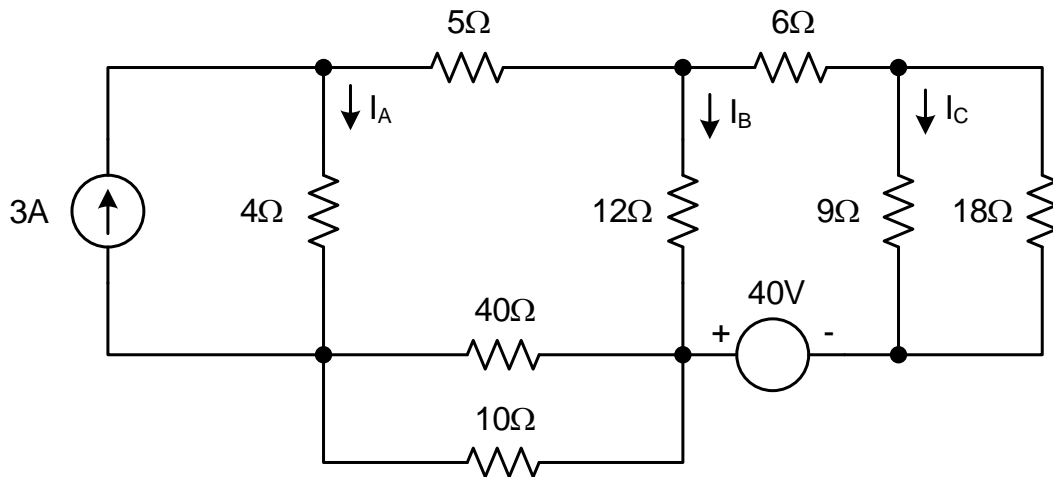2. (20) Find I_A , I_B , and I_C in the network below. Find the power for the 3 A source.



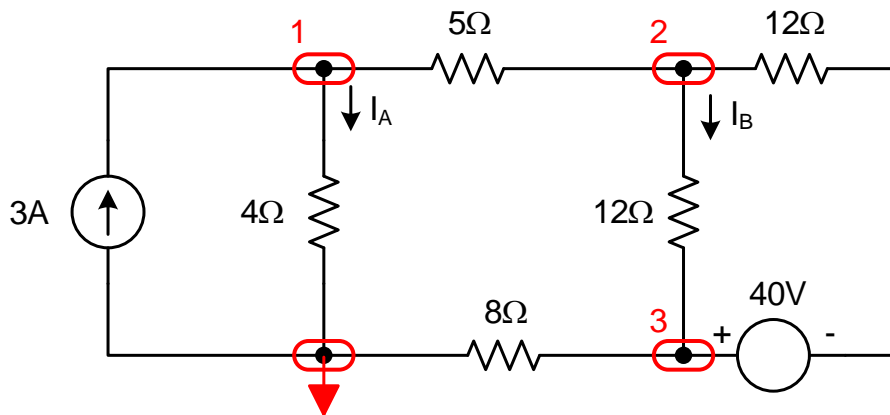Solution. We can start by simplifying the circuit. (We can combine parallel and series resistances to reduce the number of essential nodes from six to four.)



Node voltage method using V, Ω , and A.

$$1. -3 + \frac{V_1}{4} + \frac{V_1 - V_2}{5} = 0$$

$$2. \frac{V_2 - V_1}{5} + \frac{V_2 - V_3}{12} + \frac{V_2 + 40 - V_3}{12} = 0$$

$$3. \frac{V_3}{8} + \frac{V_3 - V_2}{12} + \frac{V_3 - 40 - V_2}{12} = 0$$

$$1. -60 + 5V_1 + 4V_1 - 4V_2 = 0$$

$$2. 12V_2 - 12V_1 + 5V_2 - 5V_3 + 5V_2 + 200 - 5V_3 = 0$$

$$3. 3V_3 + 2V_3 - 2V_2 + 2V_3 - 80 - 2V_2 = 0$$

$$\begin{bmatrix} 9 & -4 & 0 \\ -12 & 22 & -10 \\ 0 & -4 & 7 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ -200 \\ 80 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 6.43V \\ -0.522V \\ 11.13V \end{bmatrix}$$


$$I_A = \frac{V_1}{4\Omega} = 1.61A$$

$$I_B = \left(\frac{V_2 - V_3}{12\Omega} \right) = -0.971A$$

$$I_C = \left(\frac{V_2 + 40 - V_3}{12\Omega} \right) \left(\frac{18\Omega}{9\Omega + 18\Omega} \right) = 1.575A$$

$$P_{3A} = -(3A)V_1 = -19.29 \text{ W}$$

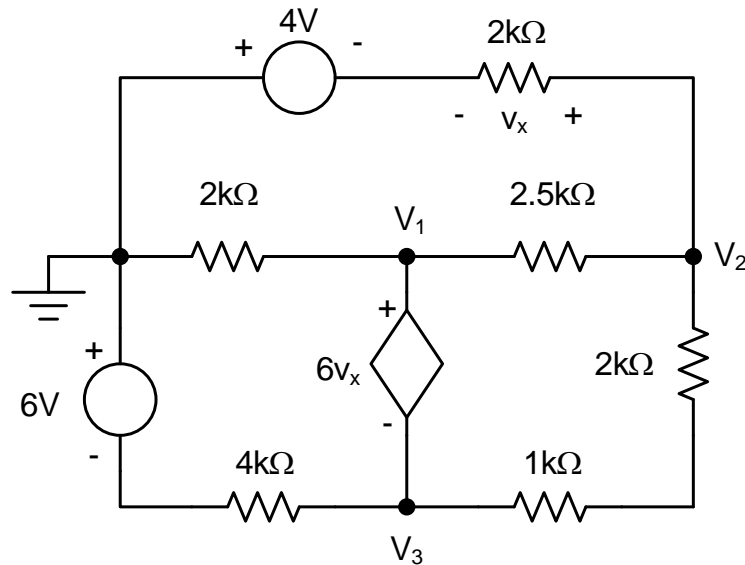3. (20) Determine V_1 , V_2 , and V_3 with respect to ground. Find v_x and the power for the dependent source.



Solution. Node voltage method using V, kΩ, and mA.

$$13. \frac{V_1}{2} + \frac{V_1 - V_2}{2.5} + \frac{V_3 + 6}{4} + \frac{V_3 - V_2}{3} = 0$$

$$2. \frac{V_2 - V_1}{2.5} + \frac{V_2 - V_3}{3} + \frac{V_2 + 4}{2} = 0$$

$$DS. V_1 - V_3 = 6V_x = 6(V_2 + 4) \quad V_1 - 6V_2 - V_3 = 24$$

$$13. 30V_1 + 24V_1 - 24V_2 + 15V_3 + 90 + 20V_3 - 20V_2 = 0$$


$$2. 12V_2 - 12V_1 + 10V_2 - 10V_3 + 15V_2 + 60 = 0$$

$$\begin{bmatrix} 54 & -44 & 35 \\ 1 & -6 & -1 \\ -12 & 37 & -10 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -90 \\ 24 \\ -60 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -1.133V \\ -3.35V \\ -5.03V \end{bmatrix}$$

$$V_x = V_2 + 4V = 0.65V$$

$$P_{6V_x} = 6V_x \left(\frac{0 - V_1}{2k\Omega} + \frac{V_2 - V_1}{2.5k\Omega} \right) = -1.25mW$$

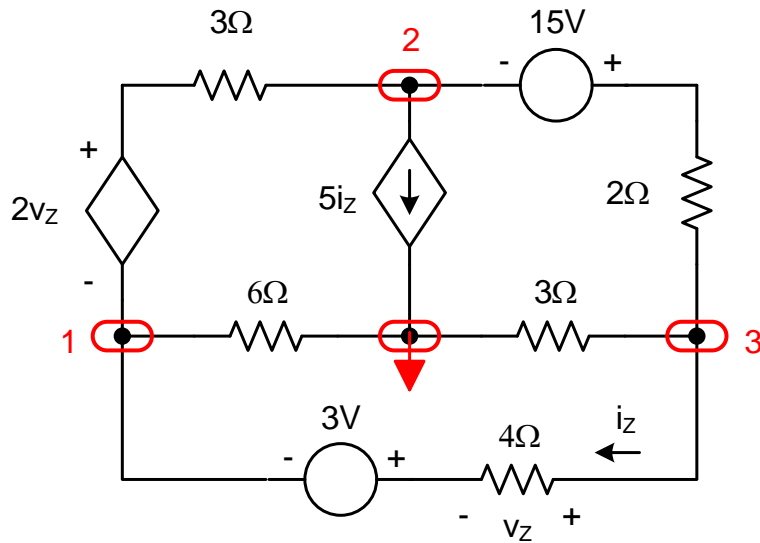4. (20) For the circuit shown, find i_z and the power for each of the sources.



Solution. Node voltage method with V, Ω , and A.

$$1. \frac{V_1 + 2v_z - V_2}{3} + \frac{V_1}{6} + \frac{V_1 + 3 - V_3}{4} = 0$$

$$2. \frac{V_2 - 2v_z - V_1}{3} + 5i_z + \frac{V_2 + 15 - V_3}{2} = 0$$

$$3. \frac{V_3 - 3 - V_1}{4} + \frac{V_3}{3} + \frac{V_3 - 15 - V_2}{2} = 0$$

$$\text{DS1. } i_z = \frac{V_3 - 3 - V_1}{4}$$

$$\text{DS2. } v_z = V_3 - 3 - V_1$$

$$1\text{DS2. } \frac{V_1 + 2(V_3 - 3 - V_1) - V_2}{3} + \frac{V_1}{6} + \frac{V_1 + 3 - V_3}{4} = 0$$

$$2\text{DS1DS2. } \frac{V_2 - 2(V_3 - 3 - V_1) - V_1}{3} + 5\left(\frac{V_3 - 3 - V_1}{4}\right) + \frac{V_2 + 15 - V_3}{2} = 0$$

$$1\text{DS2. } 4V_1 + 8V_3 - 24 - 8V_1 - 4V_2 + 2V_1 + 3V_1 + 9 - 3V_3 = 0$$

$$2\text{DS1DS2. } 4V_2 - 8V_3 + 24 + 8V_1 - 4V_1 + 15V_3 - 45 - 15V_1 + 6V_2 + 90 - 6V_3 = 0$$

$$3. 3V_3 - 9 - 3V_1 + 4V_3 + 6V_3 - 90 - 6V_2 = 0$$

$$\begin{bmatrix} 1 & -4 & 5 \\ -11 & 10 & 1 \\ -3 & -6 & 13 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 15 \\ -69 \\ 99 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -86.1V \\ -96.0V \\ -56.6V \end{bmatrix}$$

$$i_z = \frac{V_3 - 3V - V_1}{4\Omega} = 6.62A$$

$$v_z = V_3 - 3V - V_1 = 26.5V$$


$$P_{2vz} = \left(\frac{V_2 - 2v_z - V_1}{3\Omega} \right) (2v_z) = -1111W$$

$$P_{5iz} = (V_2)(5i_z) = -3180W$$

$$P_{15V} = \left(\frac{V_3 - 15V - V_2}{2\Omega} \right) 15V = 183W$$

$$P_{3V} = \left(\frac{V_3 - 3V - V_1}{4\Omega} \right) 3V = 19.88W$$

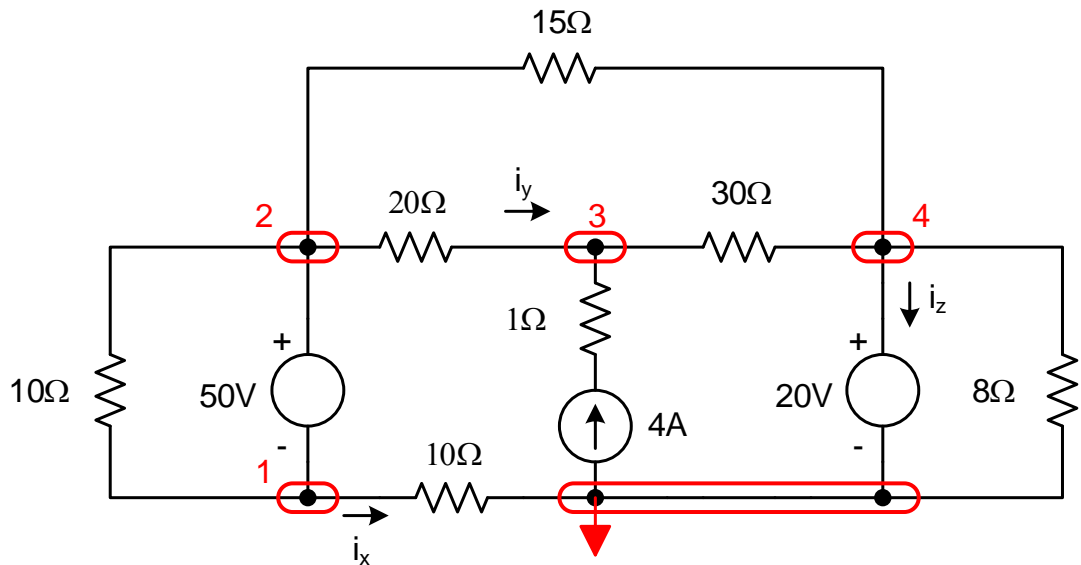5. (20) For the circuit shown, find i_x , i_y , and i_z . Find the power for the 50V source. Find the power for the 4A source.



Solution. Node voltage method using V, Ω , and A.

4. $V_4 = 20V$ (known node voltage)

12. $\frac{V_1}{10} + \frac{V_2 - 20}{15} + \frac{V_2 - V_3}{20} = 0$ (supernode)

3. $\frac{V_3 - V_2}{20} - 4 + \frac{V_3 - 20}{30} = 0$

VS. $V_2 - V_1 = 50 \quad V_1 = V_2 - 50$

12VS. $\frac{V_2 - 50}{10} + \frac{V_2 - 20}{15} + \frac{V_2 - V_3}{20} = 0$

12VS. $6V_2 - 300 + 4V_2 - 80 + 3V_2 - 3V_3 = 0$

3. $3V_3 - 3V_2 - 240 + 2V_3 - 40 = 0$

$$\begin{bmatrix} 13 & -3 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 380 \\ 280 \end{bmatrix} \quad \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 48.9V \\ 85.4V \end{bmatrix} \quad V_1 = V_2 - 50V = -1.071V$$

$$i_x = \frac{V_1}{10\Omega} = -0.1071A \quad i_y = \frac{V_2 - V_3}{20\Omega} = -1.821A$$

$$i_z = \frac{0 - V_4}{8\Omega} + \frac{V_3 - V_4}{30\Omega} + \frac{V_2 - V_4}{15\Omega} = 1.607A$$

$$P_{50V} = (50V) \left(\frac{V_1 - V_2}{10\Omega} + \frac{V_4 - V_2}{15\Omega} + \frac{V_3 - V_2}{20\Omega} \right) = -255W$$

$$P_{4A} = -(4A)(V_3 + (4A)(1\Omega)) = -357W$$